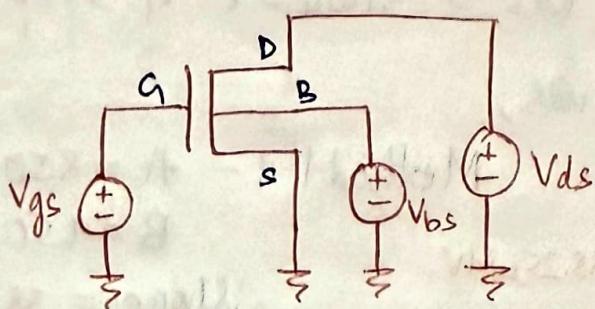


AICD - Exp 1

NMOS $\rightarrow W = 2 \mu m$

$L = 180 nm$

i) Rig up the circuit as shown.



For V_{gs} , V_{bs} , $V_{ds} \rightarrow$ Select DC voltage (V_{dc}) & assign values as V_{gs} , V_{bs} & V_{ds}


ii) Find I_D vs V_{gs} \rightarrow To find g_m \rightarrow Because $g_m = \frac{\partial I_D}{\partial V_{gs}}$

Now, ADEL \rightarrow Under Design variables column \rightarrow Right click \rightarrow Copy from cellview. $V_{bs} = 0$ $V_{ds} = 0.9 V$ $V_{gs} = 0.9 V$ $\left[\because \frac{V_{dd}}{2} = \frac{1.8}{2} = 0.9 \right]$

Now, DC analysis \rightarrow Same DC operating point \rightarrow Component parameter \rightarrow Select component \rightarrow Select V_{gs} \rightarrow Start = 0 Stop = 1.8

Outputs \rightarrow Select the drain terminal of NMOS \rightarrow Run

We get a graph as,

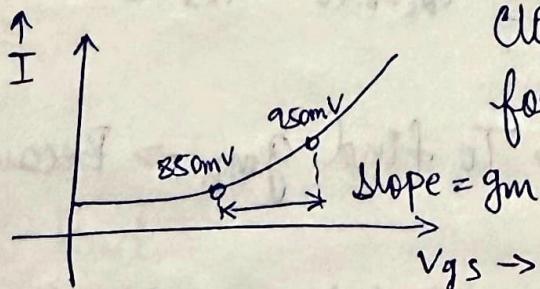


Method 1
Clock A for 1st pt & B for 2nd pt, $A = 850 mV$ & $B = 950 mV$
 \hookrightarrow Method 1

Method 2 :-

Tools \rightarrow Calculator \rightarrow Select the wave option \rightarrow Click on the above waveform \rightarrow Select the deriv function \rightarrow Evaluate the expression

We get the graph as,

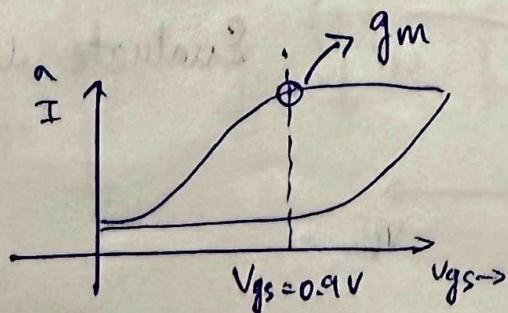


Now \rightarrow Press $V \rightarrow$ Place at $V_{gs} = 0.9 V$

$$\therefore g_m = 906.95 \mu A/V$$

3) Find I_D vs V_{ds} \rightarrow To find g_{lo} \rightarrow Because $g_{lo} = \frac{1}{\lambda I_D} = \frac{\partial V_{ds}}{\partial I_D}$ \downarrow slope

Now, DC analysis \rightarrow Select V_{ds} \rightarrow Start = 0 & Stop = 1.8V
and run, we get the graph as,

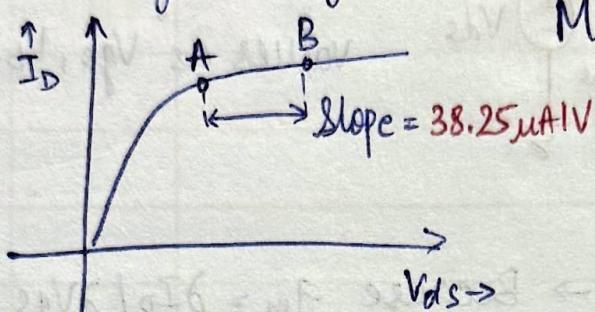

Method 1 :- $A = 850\text{mV}$


$B = 950\text{mV}$

$$\text{Slope} = 38.25 \mu\text{A/V}$$

$$1/\text{slope} = g_{lo} = 26.14\text{k}\Omega$$

Method 2 :-

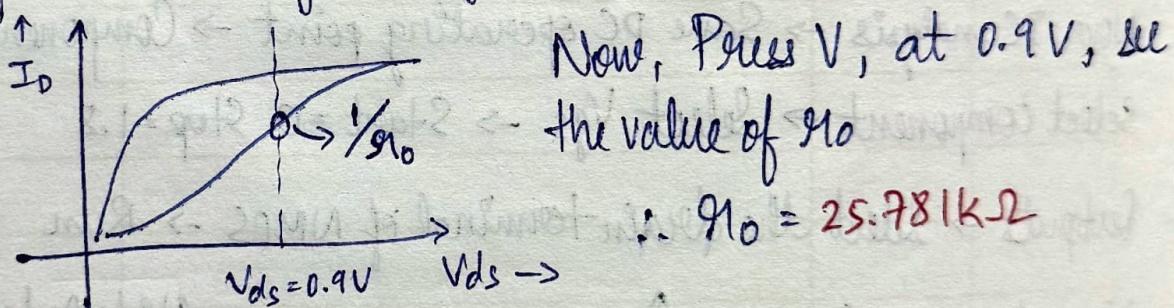Select the wave \rightarrow Apply deriv function \rightarrow Now apply $1/x$ for the deriv function, we get the graph as,




Now, Press V, at 0.9V, see the value of g_{lo}


$$\therefore g_{lo} = 25.78\text{k}\Omega$$

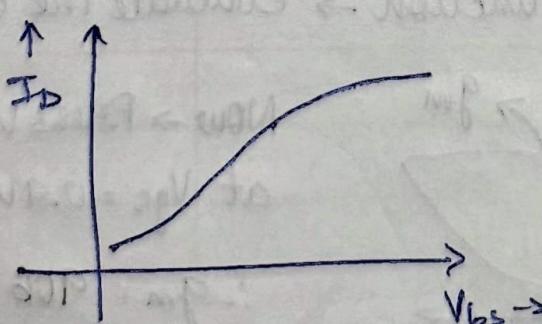a) Find I_D vs V_{bs} \rightarrow To find g_{mb} \rightarrow Because $g_{mb} = \frac{\partial I_D}{\partial V_{bs}}$

Now, DC analysis \rightarrow Select V_{bs} \rightarrow Start = -1V & Stop = +1V
and run, we get the graph as,



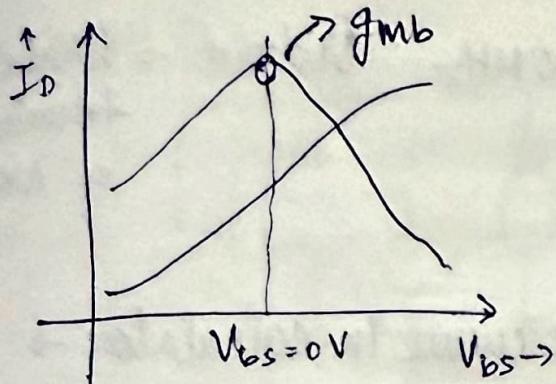Select the wave \rightarrow Apply deriv \rightarrow Evaluate, we get the graph as,



Now, Press V, at 0 V, see the value of g_{m_b} .

$$\therefore g_{m_b} = 271.5002 \mu A/V$$

5) Dummy DC analysis

Just run DC analysis \rightarrow Same DC operating points \rightarrow OK

Outputs \rightarrow Select the drain terminal of NMOS \rightarrow Run

Now, ADEL window \rightarrow Results \rightarrow Point \rightarrow DC operating points \rightarrow Click on the NMOS. Now, from the results window,

$$g_m = 917.516 \mu A/V$$

$$g_{m_b} = 276.508 \mu A/V$$

$$g_{l_D} = g_{Lout} = 26.186 K\Omega$$


$$I_D = 247.222 \mu A$$

6) AC analysis \rightarrow To get R_{out}

i) Figure :-

$$V_{DS} = 0V$$

$$V_{GS} = 0.9V$$

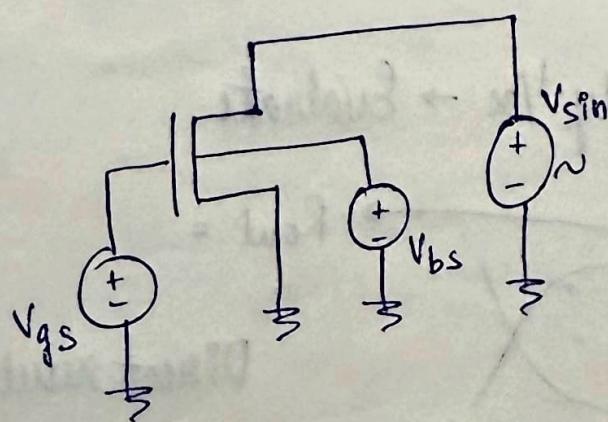

$V_{Ssin} \rightarrow$ DC voltage = 0.9 V


AC mag = 1 V

$V_{BS} \& V_{GS} \rightarrow V_{DC}$

Note :- Remember to remove the V_{DS} Variable in ADEL window

Now, AC analysis \rightarrow Frequency \rightarrow 1 to 100 MHz Output \rightarrow Drain terminal of NMOS


We get the curve as.

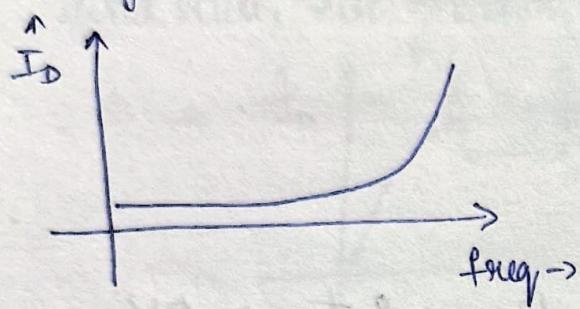

Now, Select the curve in calculator \rightarrow
Apply the $1/x$ function \rightarrow Evaluate

Now, we get the curve as.

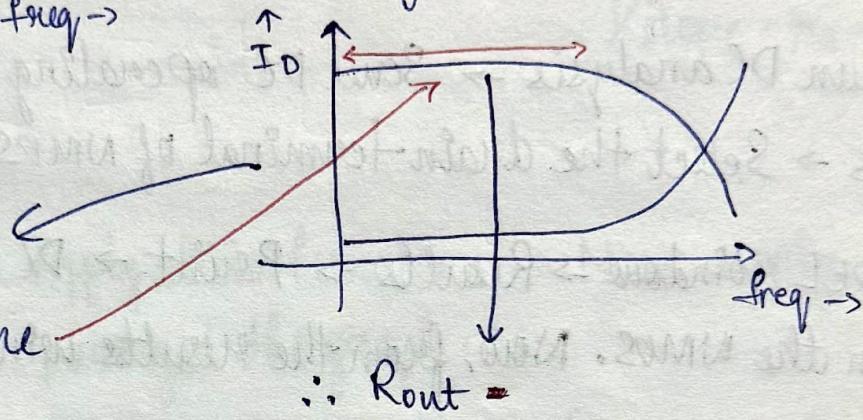
Simply place the cursor on the top most curve, anywhere on the straight line



$$\therefore R_{out} =$$

ii) Figure 2 :-

$$w = 2\mu \\ L = 180n$$

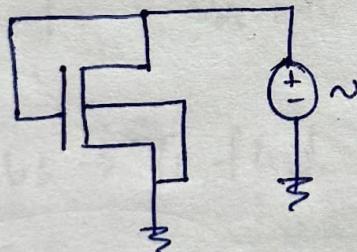


$$V_{sin} \rightarrow \text{DC voltage} = 0.9V \\ \text{AC mag} = 1V$$

Outputs \rightarrow Drain of NMOS

AC analysis \rightarrow Freq = 1 to 100 MHz

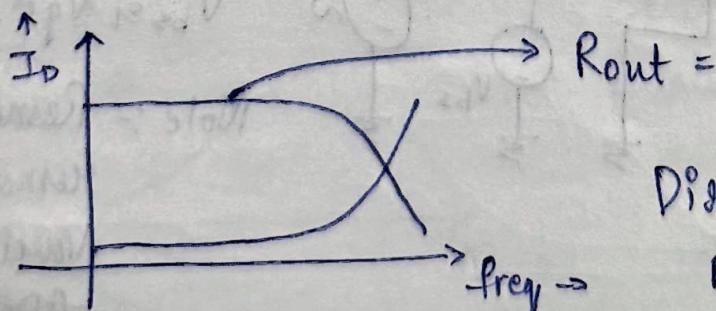
We get a curve \rightarrow Apply $1/x$ \rightarrow Evaluate



Direct result,

$$R_{out} = \frac{1}{g_m} \parallel R_o$$

iii) Figure 3 :-

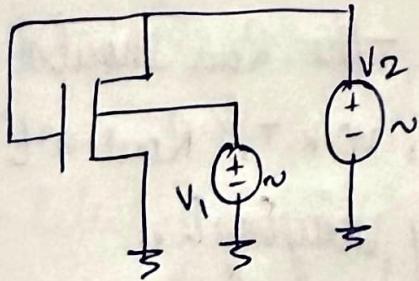


$V_1 \rightarrow V \sin \theta \rightarrow$ DC voltage = 0V

AC mag = 1V

$V_2 \rightarrow V \sin \theta \rightarrow$ DC voltage = 0.9V

AC mag. = 1V

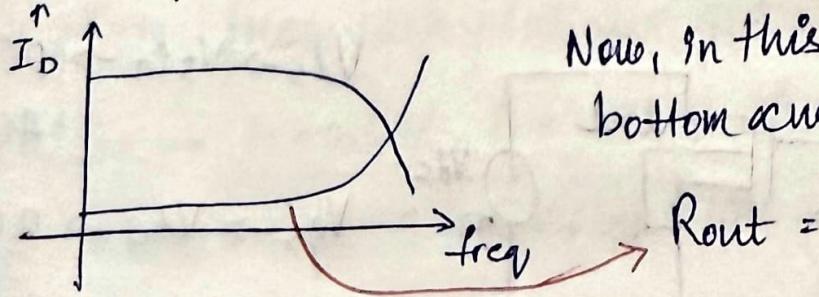AC analysis \rightarrow Freq. = 1 to 100MHz \rightarrow Select the curve \rightarrow Apply $1/x$



Now, in this figure, select the bottom curve and find R_{out} .

$$R_{out} =$$


Now, Direct result, $R_{out} = \frac{1}{g_m + g_{mb}} \text{ II } 91\Omega$

AICD - Exp2

Theoretically, for a current mirror, the Rout should be ideally ∞ and practically as high as possible. W.K.T., $Rout \propto L$, therefore we need to determine the Rout value by varying L.

i) Rig up circuit as below,

$$W = 10\mu$$

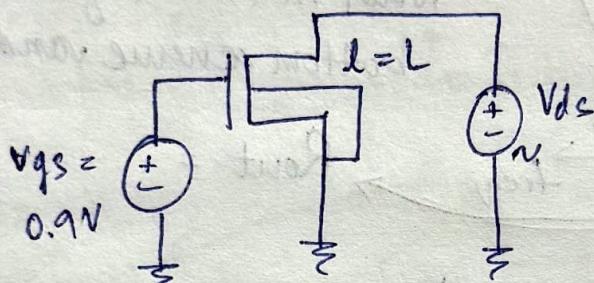

$$V_{ds} \rightarrow V_{sin} \rightarrow \text{DC voltage} = 0.9V$$

$$\text{AC mag} = 1V$$

$$V_{gs} \rightarrow V_{de} \rightarrow \text{DC voltage} = 0.9V$$

$$L = 180\text{nm}, 590\text{nm}, 1\mu\text{m}$$


(vary the length)

W.K.T., to get Rout, we do AC analysis with $f = 1$ to 1GHz .

In ADEL window → Design variables → Right click → Copy from cellvalue

Perform three trials with $L = 180\text{nm}, 590\text{nm}, 1\mu\text{m}$

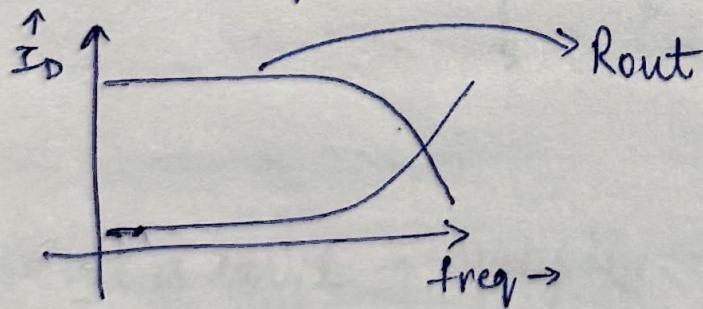Run AC analysis → Select the curve → Apply $1/x$ function → Evaluate



	Rout
180nm	5.72k Ω
590nm	52.54k Ω
1 μm	118.28k Ω

We select the value of L for which


Rout is ∞ .

$$\therefore L = 1\mu\text{m}$$


Now,
 Analyses \rightarrow DC \rightarrow Save DC operating points \rightarrow Component parameter \rightarrow
 select component \rightarrow Select V_{ds} \rightarrow DC voltage \rightarrow Start = 0, Stop = 1.8
 Outputs \rightarrow Select the NMOS drain terminal
 Now, run parameter analysis \rightarrow Variable = L, Start = 180 nm,
 Stop = 1 μm, Mode = Auto, Steps = 3 \rightarrow Run
 we get three plots, from each plot we get I_D variation & R_o
 For I_D variation \rightarrow A = 0.5 V, B = 1.8 V, check the dy value
 For R_o \rightarrow A = 850 mV, B = 950 mV, get the slope value δ_1

$$R_o = 1/\text{slope}$$

L	dy = I_D variation	R_o
180 nm	220.98 μA	5.714 kΩ
590 nm	24.943 μA	52.33 kΩ
1 μm	11.886 μA	117.7 kΩ

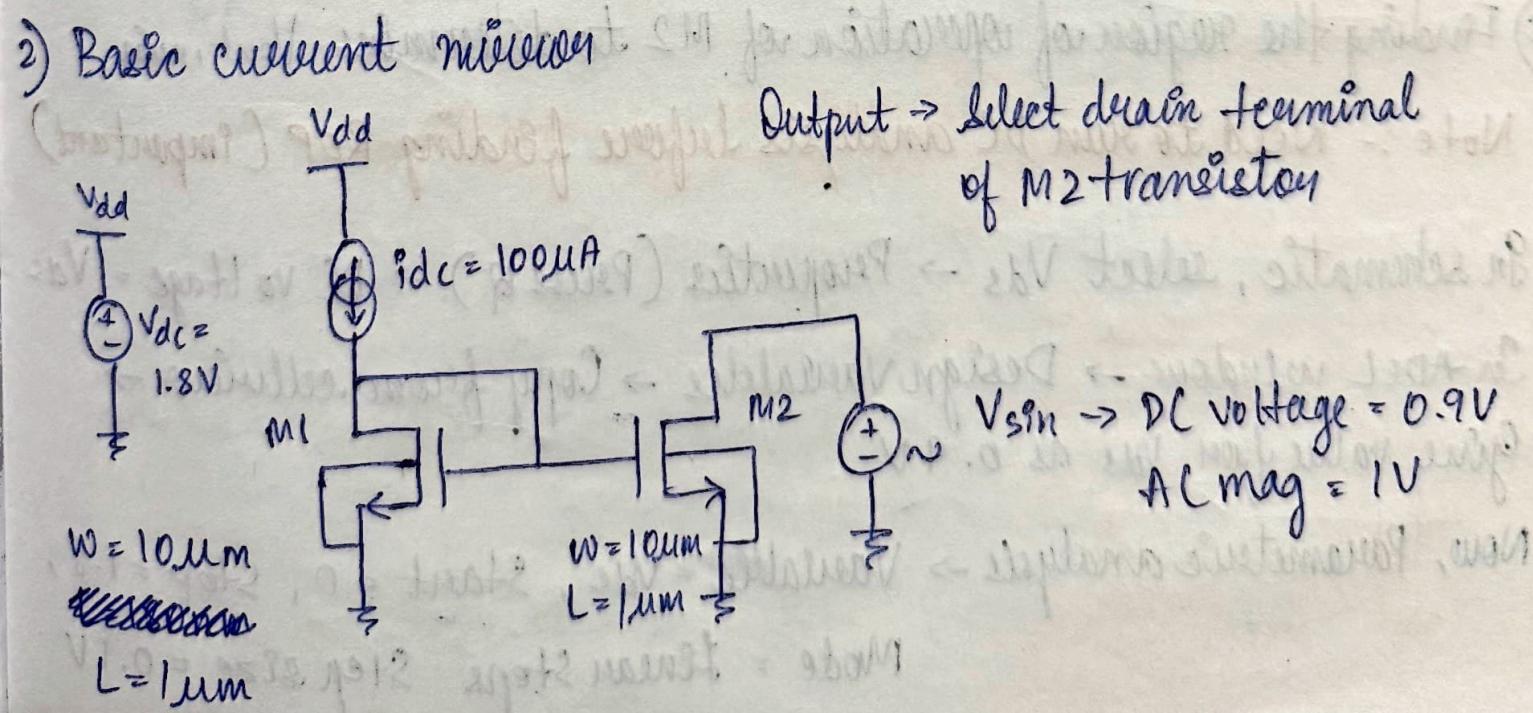


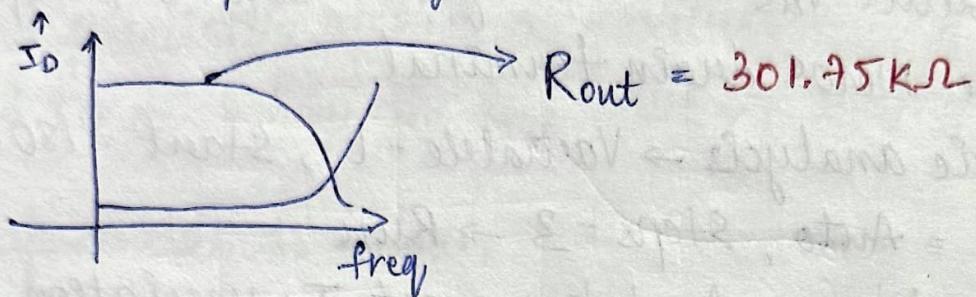a) AC analysis \rightarrow Freq = 1 to 1 GHz \rightarrow Run \rightarrow Select the schematic calculator by enabling wave option \rightarrow Apply $1/x$ function \rightarrow Evaluate



$$R_{out} = 301.75 \text{ k}\Omega$$

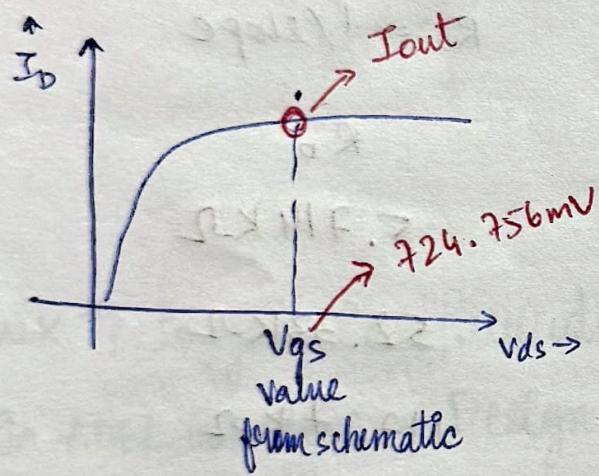b) DC analysis \rightarrow Select component \rightarrow Select V_{ds} \rightarrow Start = 0 Stop = 1.8



Now in the schematic, check what is the value of V_{gs} for M2 transistor. So from that V_{gs} value, check what is the I_D value in DC analysis.

$$\therefore I_{out} = 99.9996 \text{ mA}$$

c) Finding the region of operation of M2 to determine $V_{out,min}$

Note :- Need to run DC analysis before finding ROP (Important)


In schematic, select V_{ds} \rightarrow Properties (Press Q) \rightarrow DC voltage = V_{ds}

In ADEL window \rightarrow Design Variables \rightarrow Copy from cellview \rightarrow Give value for V_{ds} as 0.9 V

Now, Parametric analysis \rightarrow Variable = V_{ds} , Start = 0, Stop = 1.8,

Mode = Linear Step Step size = 0.1 V

We get the graph as,

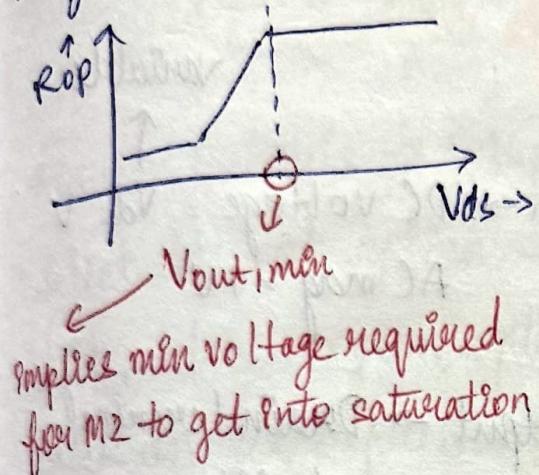

Get the value for $V_{out,min}$ where the value of $R_{op} = 2$.

$$\therefore V_{out,min} = 0.3V$$

Now, for the value of $V_{out,min} = 0.3V$ check what is the current value in the DC source.

Check if both I_{out} & I_D value at $V_{out,min}$ are very close or similar which justifies the current mirror operation.


Note :- Before parametric analysis, do the following (mandatory)

Outputs \rightarrow Setup \rightarrow Name = R_{op} \rightarrow Calculator Open \rightarrow select the Opt option \rightarrow In schematic select M2 \rightarrow In the dialogue box \rightarrow Click on list \rightarrow Select region \rightarrow

Now, go back to the setup window \rightarrow Select Get expression \rightarrow OK

$$I_D \text{ at } V_{out,min} = 95.7005 \text{ mA}$$


3) Cascode current mirror

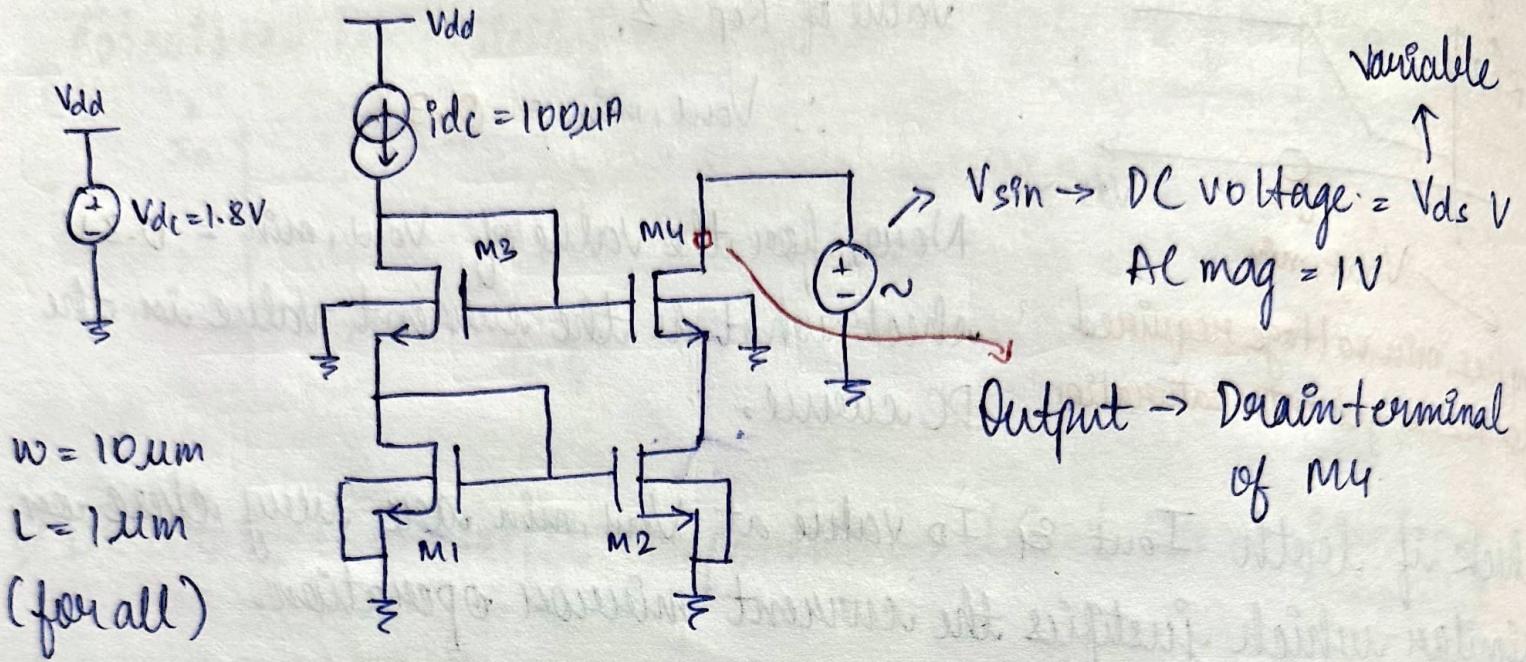

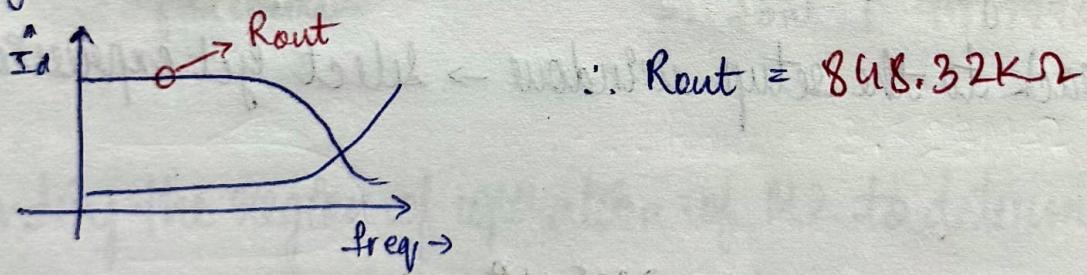
a) AC analysis \rightarrow Freq = 1 to 1 GHz \rightarrow OK

Output \rightarrow Drain of M_4

ADEL \rightarrow Design variables \rightarrow Right click \rightarrow Copy from cellview \rightarrow Give $V_{ds} = 0.9V$ \rightarrow Run \rightarrow Select the curve \rightarrow Apply $Y(x)$ function \rightarrow



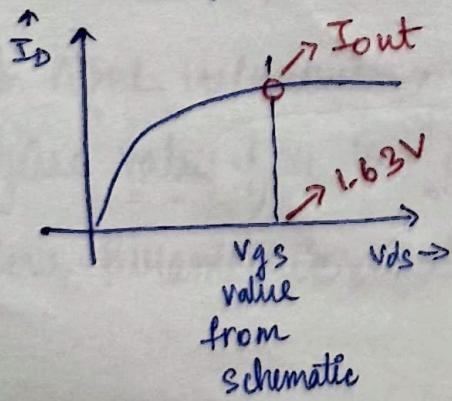b) DC analysis \rightarrow Select $V_{ds} \rightarrow$ Start = 0, Stop = 1.8V \rightarrow Run



Now, in schematic, check the V_{gs} value of M_4 transistor. For that value, check what is I_D in DC curve.

$$\therefore I_{out} = 99.99992 \mu A$$

c) Finding ROP w.r.t M2 & MU transistors, to get $V_{out,min}$
Note :- DC analysis should have been done before determining ROP.


ADEL → Outputs → Setup → Name = ROPU → Open Calculator → Select the opt option → In schematic, select MU → Under the list, select region option → None, go back to setup window → click on Get expression → OK

Do the same for value for M2 transistor → Name = ROPL

Now, Parameteric analysis → Variable = Vds, Start = 0, Stop = 1.8,
Mode = Linear steps Step size = 0.1

Note:- Before running parametric analysis, see to that the ROPU & ROPL under the Outputs window is enabled & the drain of MU is disabled.

Run → We get a curve as,

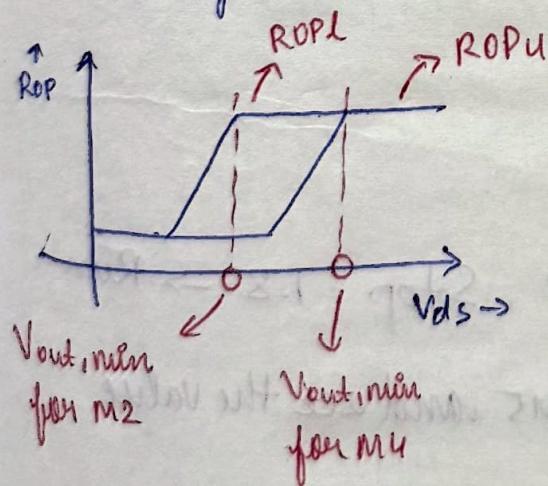


$$V_{out,min}(MU) = 1V$$

Now, for the above value, check the value of I_D in DC analysis curve & verify if this value or the I_{out} value is similar / very close.

$$I_D \text{ at } V_{out,min} = 99.97075 \mu A$$

a) Low voltage cascode current mirror

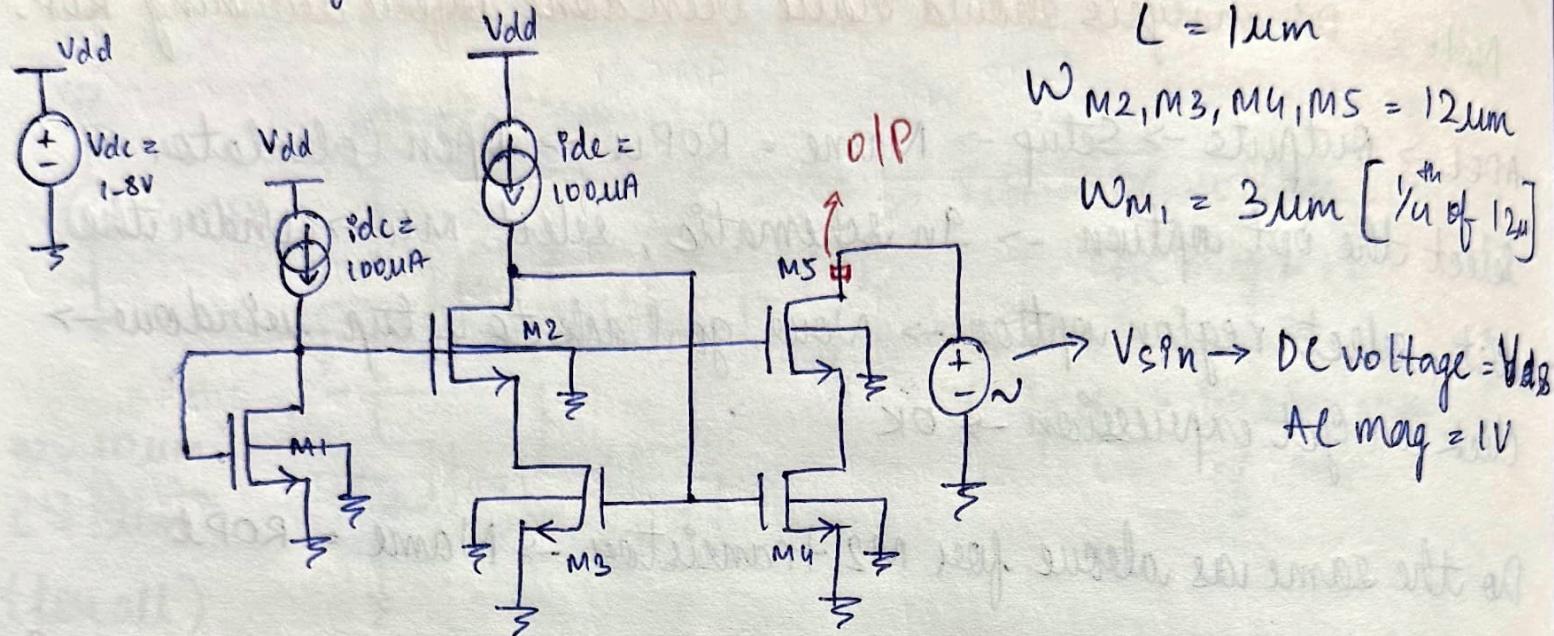


a) AC analysis $\rightarrow f = 1$ to 1 GHz


Output \rightarrow Drain terminal of M5

ADEL \rightarrow Design variables \rightarrow Copy from cellview $\rightarrow V_{ds} = 0.9V \rightarrow$ Run

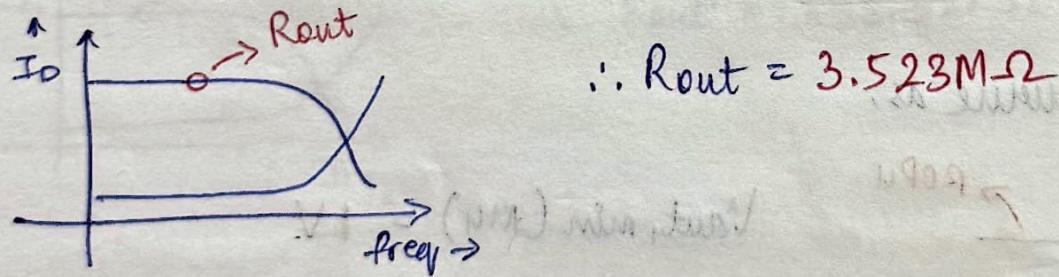Select the curve \rightarrow Apply $1/n$ function \rightarrow Evaluate



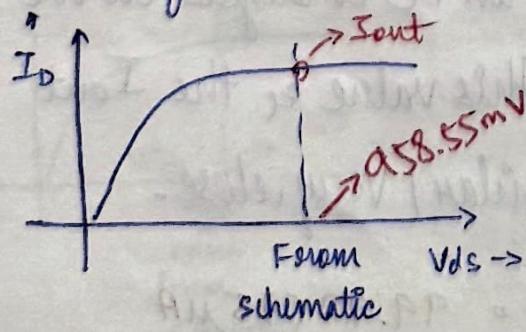b) DC analysis \rightarrow Select $V_{ds} \rightarrow$ Start = 0, Stop = 1.8 \rightarrow Run



Check V_{gs} of M5 and see the value of I_{ds}

$$\therefore I_{out} = 100.102mA$$


c) Finding ROP of M5 & M4

ADEL → Outputs → Setup → Name = ROPu → Open calculator → Select opt → Click on M5 → Select region → From the setup window → Click on Get Expression → OK

Do the same for transistor M4 → Name = ROPd

Run parametric analysis → Variable = Vds, Start = 0, Stop = 1.8, Mode = Linear steps Step size = 0.1

We get the curve as,

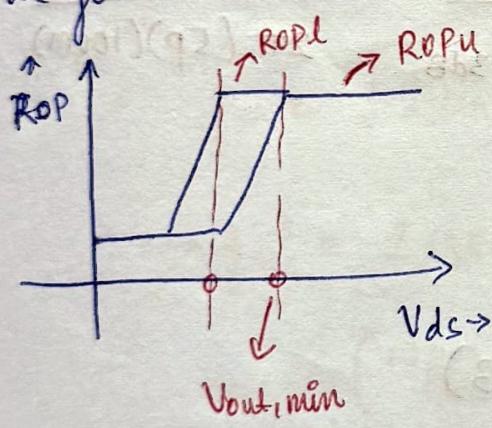

$$\therefore V_{out,min}(M5) = 0.5V$$

Check Id value vs the value of Id at $V_{out,min}$ in the DC curve.

$$I_D \text{ at } V_{out,min} = 99.8037 \text{ mA}$$



$$V_{out,f,21} = \frac{2}{2-212} = 0.826 \text{ V}$$

$$V_{2,0} = 0.826 \text{ V}$$

$$V_{3,0} = 0.636 \text{ V}$$

$$V_{2,1} = 0.8 - 0.636 = 0.164 \text{ V}$$

AICD - Exp 3(a)

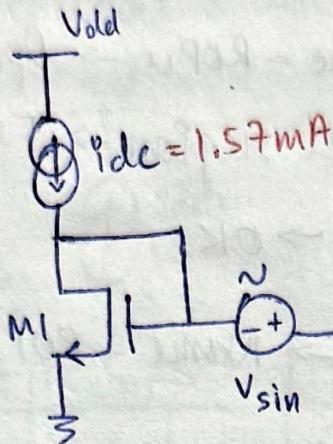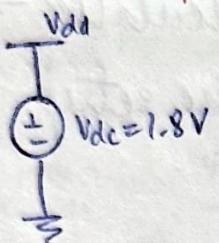

$V_{\text{sin}} \rightarrow \text{AC mag} = 1V$
 $\text{freq} = 1\text{KHz}$
 $\Delta \text{Vpp} = 1\text{mV}$

$F_W = 0.45\mu\text{m}$
 $F = 5$
 $T_W = 202.25\mu\text{m}$
 $L = 1\mu\text{m}$

Let $V_{\text{DD}} = 1.8\text{V}$, $|A_V| = 5$, $f_{3\text{dB}} = 100\text{MHz}$, $C_L = 5\text{pF}$

$$\text{W.K.T, } f_{3\text{dB}} = \frac{1}{2\pi R_L C_L} \Rightarrow R_L = \frac{1}{2\pi C_L f_{3\text{dB}}} = \frac{1}{2\pi (5\text{p})(100\text{m})}$$

$$\therefore R_L = 318.3\Omega$$

W.K.T,

$$|A_V| = g_m R_L \Rightarrow 5 = g_m (318.3)$$

$$\therefore g_m = \frac{5}{318.3} = 15.7\text{mA/V}$$

To find operation region of T^* , run a dummy DC analysis, keep the default values of T^* & $i_{\text{dc}} = 100\text{mA}$, $R_L = 318.3\Omega$, $C_L = 5\text{pF}$. Default $T^* \Rightarrow W = 1\mu\text{m}$ $L = 180\text{nm}$, $F = 1$, $M = 1$. Now, from the Point Results \rightarrow DC operating points, get values of V_{gs} & V_{th} .

$$\therefore V_{\text{gs}} = 730.753\text{m} \simeq 0.8\text{V}$$

$$V_{\text{th}} = 542.767\text{m} \simeq 0.6\text{V}$$

$$\therefore V_{\text{ov}} = V_{\text{gs}} - V_{\text{th}} = 0.8 - 0.6 = 0.2\text{V}$$

$$\text{Now, } I_D = \frac{1}{2} \mu_{n\text{Cox}} (W/L) (V_{gs} - V_{th})^2 = \frac{1}{2} \underbrace{\mu_{n\text{Cox}} (W/L)}_{g_m} \underbrace{(V_{gs} - V_{th})(V_{gs} - V_{th})}_{V_{ov}}$$

$$\therefore I_D = \frac{1}{2} g_m V_{ov} = \frac{1}{2} (15.7m)(0.2) = 1.57 \text{ mA}$$

$$\boxed{\therefore I_{dc} = 1.57 \text{ mA}}$$

Now, to find W/L

$$\text{For } 180 \text{ nm} \rightarrow \mu_{n\text{Cox}} = 388.125 \text{ MA/V}^2$$

W.K.T.

$$g_m = \sqrt{2 \mu_{n\text{Cox}} (W/L) I_D}$$

$$\Rightarrow g_m^2 = 2 \mu_{n\text{Cox}} (W/L) I_D$$

$$\therefore (W/L) = \frac{g_m^2}{2 \mu_{n\text{Cox}} \cdot I_D} = \frac{(15.7m)^2}{2(388.125 \mu)(1.57m)}$$

$$\therefore \frac{W}{L} = \frac{(15.7m)(15.7m)}{2(1.57 \mu)(388.125 \mu)} = 0.20225 \frac{\text{m}}{\mu}$$

$$\therefore \frac{W}{L} = \frac{202.25 \mu}{1 \mu}$$


$$\Rightarrow \boxed{W = 202.25 \mu\text{m} \\ L = 1 \mu\text{m}}$$

Make Fingers, $F=5$ $\therefore TW = 202.25 \mu\text{m}$

$$FW = \frac{TW}{F} = \frac{202.25 \mu}{5}$$

$$\therefore FW = 40.45 \mu\text{m}$$

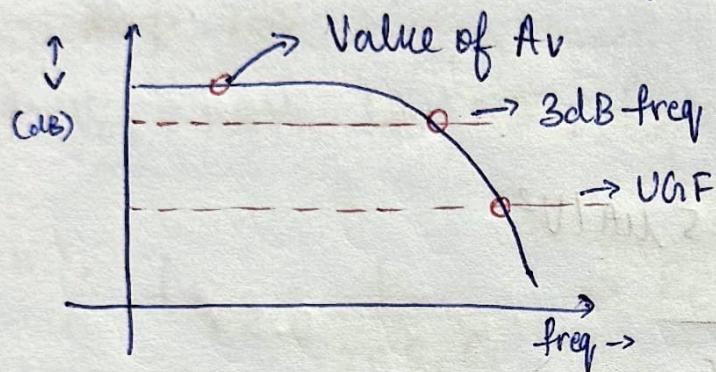1) AC analysis \rightarrow freq = 1 to 1GHz \rightarrow Just run without any o/p \rightarrow
Now in ADEL window \rightarrow Results \rightarrow Direct plot \rightarrow Main form \rightarrow
In the Direct Plot Form window \rightarrow Analysis = ac, Function =
voltage, Select = Net, Modifier = dB20 \rightarrow Select the o/p net
(Dont press on OK) \rightarrow We get the waveform.



For 3dB freq \rightarrow Check the value of Av, then at Av - 3, place a horizontal line (Press H) \rightarrow Check the freq. value


For VCF \rightarrow Place a horizontal line at 0dB \rightarrow Check the freq. value

$$\therefore Av(\text{in dB}) = 13.12$$

$$3\text{dB freq} = 95.385 \text{MHz} \text{ at } 10.12 \text{ dB}$$

$$VCF = 397.99 \text{ MHz}$$

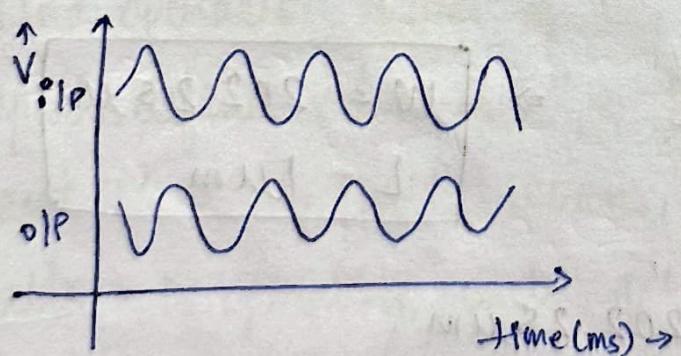2) Transient analysis \rightarrow Stop time = 10m
Outputs \rightarrow Select the o/p net & the i/p net (For M2) of V_{sin}



Now, Calculation \rightarrow Select the wave option \rightarrow Select the o/p curve \rightarrow apply Peak-to-Peak function \rightarrow Evaluate



Do the same for i/p curve

$$\therefore V_o(P-P) = 9 \text{ mV}$$

$$V_i(P-P) = 2 \text{ mV}$$

$$Av = \frac{V_o(P-P)}{V_i(P-P)} = \frac{9 \text{ m}}{2 \text{ m}} = 4.5$$

AICD - Exp 3(b)

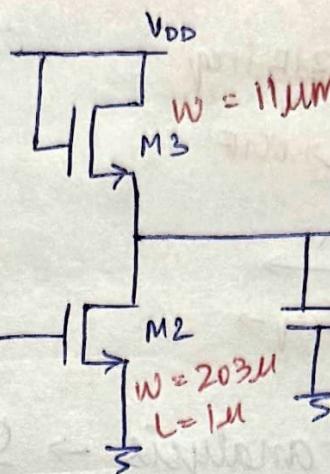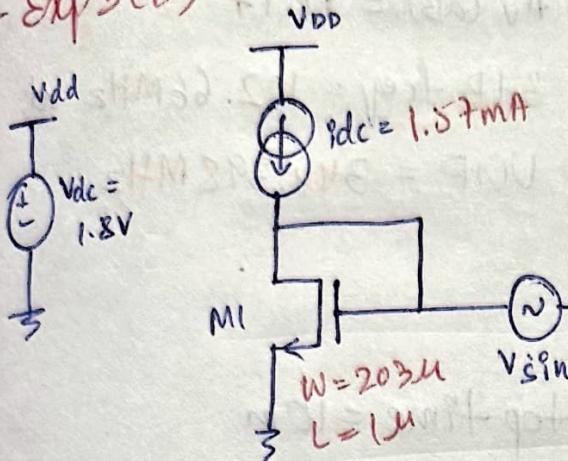

$$V_{DD} = 1.8V$$

$$|AV| = 5$$

$$f_{3dB} = 100MHz$$

$$C_L = 5pF$$

$$V_{sin} \rightarrow AC \text{ mag} = 1V$$

$$\text{Amp} = 1mV$$

$$\text{freq} = 1kHz$$

$$1.57mA$$


Now, $M_1 \& M_2 \rightarrow W/L = 203\mu/1\mu$ Initially keep $idc = \boxed{1.57mA}$

Now, run dummy DC analysis & find g_m & g_{mb} of M_3 transistor

Now, for M_3 , $L = 1\mu m$ & $w = W$ [We need to find w of M_3 such that M_2 remains in saturation].

Now, find R_{OP} of M_2 via \rightarrow ADEL \rightarrow Outputs \rightarrow Setup \rightarrow Name = R_{OP} \rightarrow Open Calculator \rightarrow Select opt option \rightarrow Click on $T^9 M_2$ \rightarrow Under list, select region \rightarrow Go to Setup window \rightarrow Click on get expression \rightarrow OK

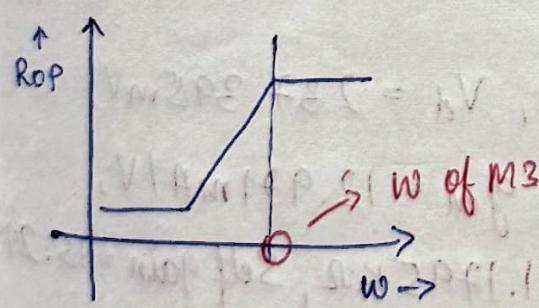
Now, run parametric analysis \rightarrow Variable = W , From = 2μ , To = 15μ , Step mode = Linear steps Size = 1μ



$$\therefore w \text{ of } M_3 = 11\mu m$$

Now, change w of M_3 and perform AC analysis \rightarrow freq = 1 to 10kHz Outputs \rightarrow Vout net \rightarrow Run the analysis \rightarrow Click on the waveform \rightarrow Right-click \rightarrow Dependent modifier \rightarrow dB20

Now,

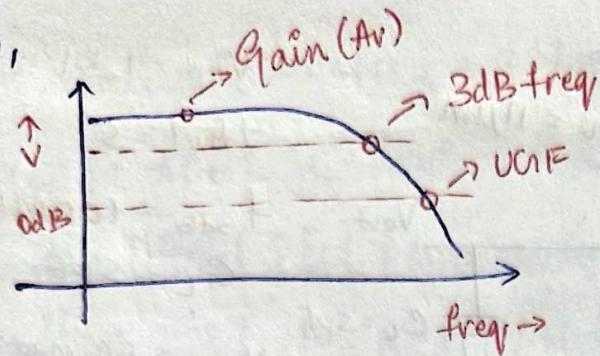


$$\therefore Av (\text{dB}) = 11.17$$

$$3\text{dB freq} = 102.66 \text{ MHz at } 8.17$$

$$UCRF = 344.398 \text{ MHz}$$

Now, perform transient analysis \rightarrow Stop time = 10 ms

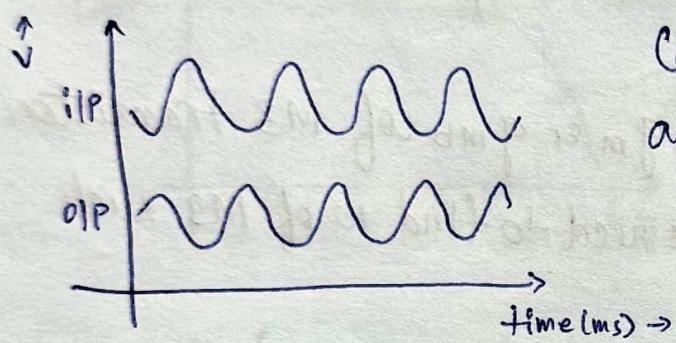Outputs $\rightarrow V_{\text{out net}}$ & S/I P net of M2



Calculator \rightarrow Select the S/I P / 0/I P waveform \rightarrow apply Peak-to-Peak function \rightarrow Evaluate

$$V_o(\text{P-P}) = 7.2 \text{ mV}$$

$$V_i(\text{P-P}) = 2 \text{ mV}$$

$$A_v = \frac{V_o(\text{P-P})}{V_i(\text{P-P})} = \frac{7.2 \text{ m}}{2 \text{ m}} = 3.6$$

Exp 3a \rightarrow M2 $\rightarrow V_g = 655.503 \text{ mV}$, $V_s = 0 \text{ V}$, $V_d = 1.28956 \text{ V}$,

$V_b = 0 \text{ V}$, $I_D = 1.606 \text{ mA}$, $g_m = 14.462 \text{ mA/V}$,

$g_{ds} = 48.4256 \text{ mA/V}$, $R_o = 20.65 \text{ k}\Omega$, Self gain = 298.64

Exp 3b \rightarrow M2 $\rightarrow V_g = 655.447 \text{ mV}$, $V_s = 0 \text{ V}$, $V_d = 237.395 \text{ mV}$,

$V_b = 0 \text{ V}$, $I_D = 1.4895 \text{ mA}$, $g_m = 12.971 \text{ mA/V}$,

$g_{ds} = 847.829 \text{ mA/V}$, $R_o = 1.1795 \text{ k}\Omega$, Self gain = 15.299

M3 $\rightarrow V_g = 1.8 \text{ V}$, $V_d = 1.8 \text{ V}$, $V_b = 237.395 \text{ mV}$, $V_b = 0 \text{ V}$,


$I_D = 1.4895 \text{ mA}$, $g_m = 2.071 \text{ mA/V}$, $g_{ds} = 25.375 \text{ mA/V}$,

$R_o = 39.41 \text{ k}\Omega$, Self gain = 81.6007


AICD - Expla

The transistors M_1 & M_2 need to be sized.
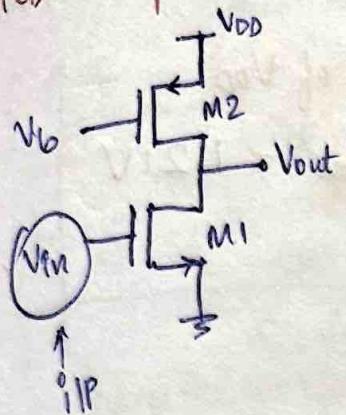
$$L = 3 \text{ times } 180 \text{ nm} \approx 500 \text{ nm}$$



Consider the figure below

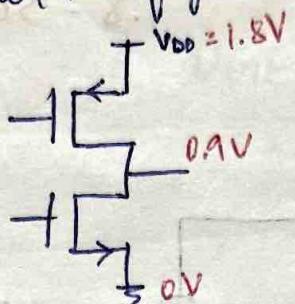


Using the Potential Divider Method (PDM), we estimate the voltage at drain of each transistor, here
 $V_{DD} = 1.8 \text{ V}$ No. of $T^r = 2$

$$\therefore V \text{ at each node} = \frac{V_{DD}}{n} = \frac{1.8}{2} = 0.9$$


Now, consider the NMOS,
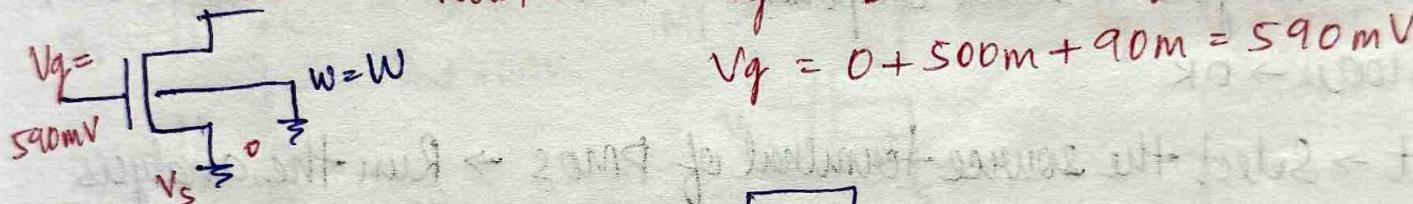
$$0.9 \quad \text{Now, W.K.T., } -V_g = V_B + V_{TH} + 5\% \text{ of } V_{DD}$$




$$V_g = 0 + 500 \text{ mV} + 90 \text{ mV} = 590 \text{ mV}$$

Now, connect the ckt as,

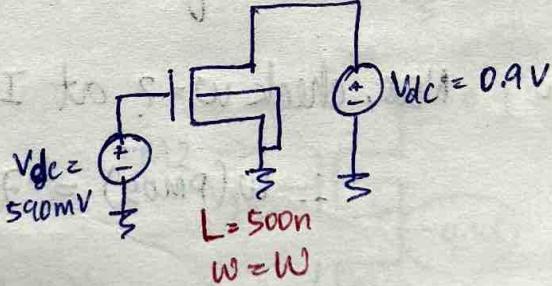


Now, DC analysis \rightarrow Same dc operating point \rightarrow Component parameters \rightarrow
 Select component \rightarrow Select the NMOS \rightarrow Select $89 \mu\text{m}W$ (simulation width) \rightarrow
 $S_{start} = 2 \mu\text{m}$, $S_{stop} = 50 \mu\text{m} \rightarrow OK$

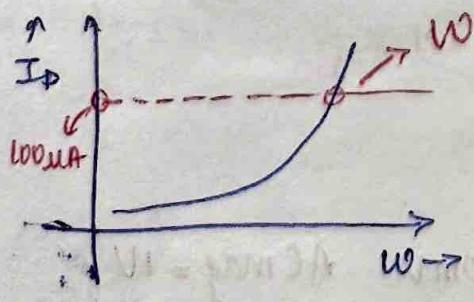Output \rightarrow Select drain of NMOS \rightarrow Run the analysis



Now, place a horizontal line (Press H) at $I_D = 100 \mu\text{A}$. Now see the value of W .
 $\therefore W = 14.373 \mu\text{m}$
 (NMOS)

Now, consider the PMOS.

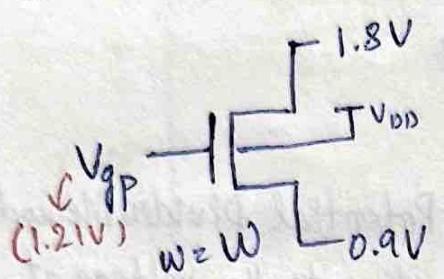


Now, W.K.T,

$$V_{gp} = V_s - (V_{thp}) - 5\% \text{ of } V_{DD}$$

$$= 1.8 - 500m - 90m = 1.21V$$


Now, connect the ckt. as,

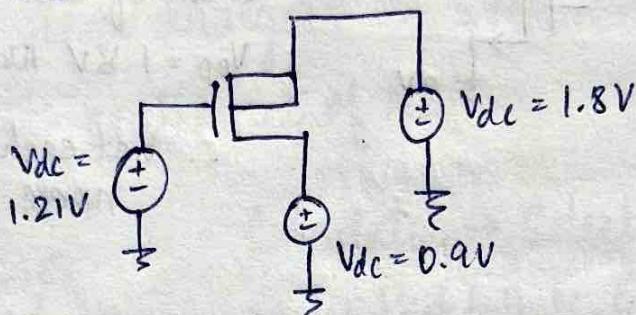

Now, DC analysis \rightarrow Select component \rightarrow PMOS \rightarrow $\sin W \rightarrow S_{act} = 2\mu$,

$$S_{act} = 100\mu \rightarrow \text{OK}$$

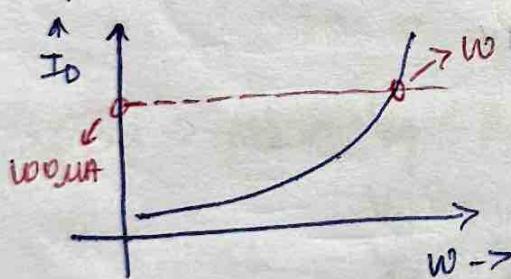
Output \rightarrow Select the source terminal of PMOS \rightarrow Run the analysis



Now, check $w = ?$ at $I = 100\mu A$


$$\therefore w(\text{PMOS}) = 73.76\mu m$$

Now, finally connect the ckt. as,

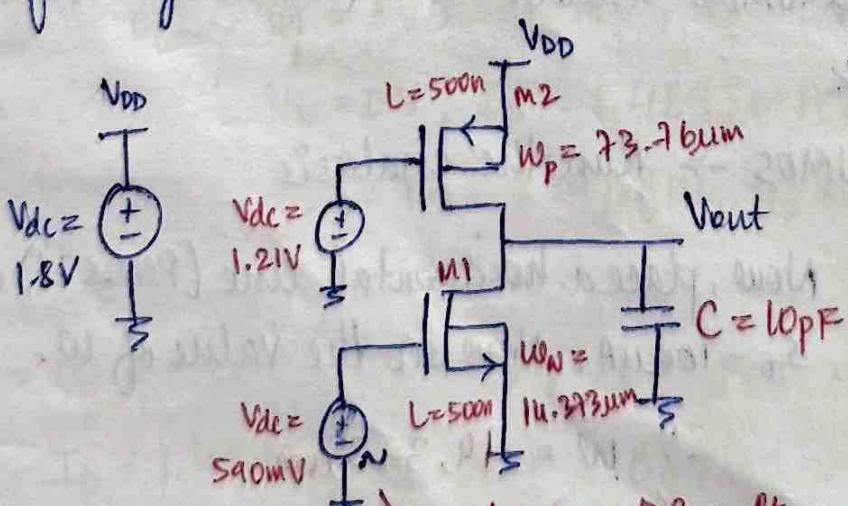

$V_{SPN} \rightarrow \text{DC voltage} = 590mV$ $Af \text{ mag} = 1V$
 $\text{freq} = 1\text{kHz}$ $\text{Amp} = 1mV$

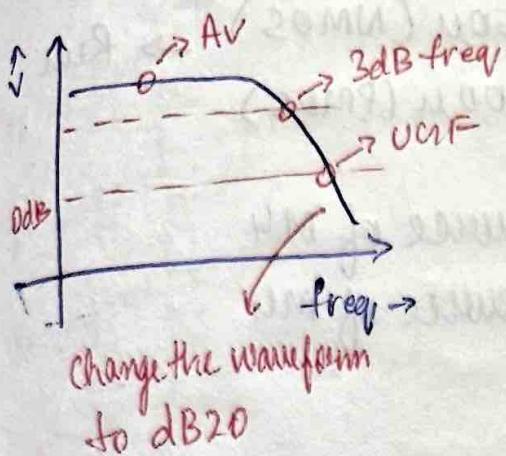Now, AC analysis \rightarrow freq = 1 to 1 GHz Output \rightarrow Vout net




$$\therefore Av(\text{dB}) = 37.84$$

3dB freq = 252.51 kHz at 34.84 dB


$$UCF = 20.153 \text{ MHz}$$

AICD - Exp 4 b

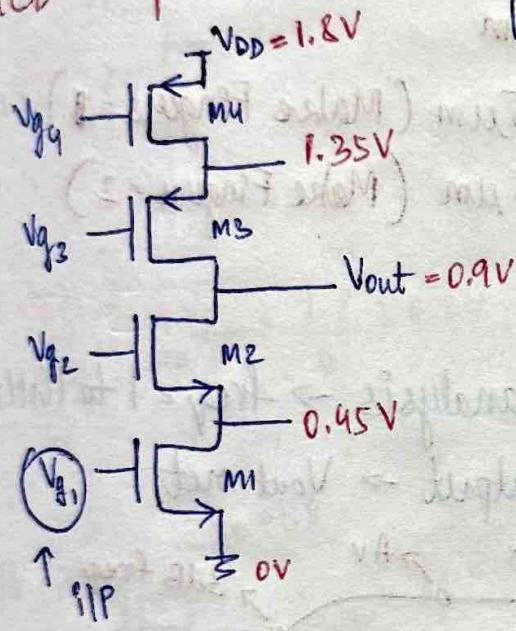


$$V_{\text{at each node}} = \frac{V_{DD}}{n} = \frac{1.8}{4} = 0.45 \text{ V}$$

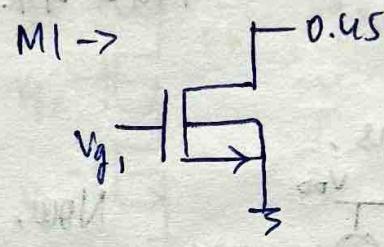We get the node voltages using PDM,
Now perform transistor sizing,



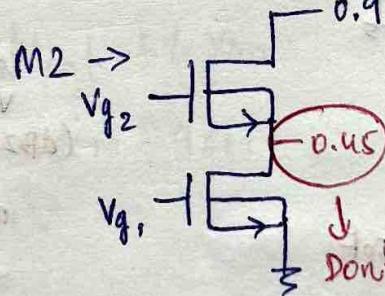
$$\begin{aligned} V_{q_1} &= V_s + V_{Th} + 5\% V_{DD} \\ &= 0 + 500 \text{ mV} + 90 \text{ mV} \\ \therefore V_{q_1} &= 590 \text{ mV} \end{aligned}$$




$$\begin{aligned} V_{q_2} &= V_s + V_{Th} + 5\% V_{DD} \\ &= 0.45 + 500 \text{ mV} + 90 \text{ mV} \\ \therefore V_{q_2} &= 1.04 \text{ V} \end{aligned}$$

Don't connect during schematic

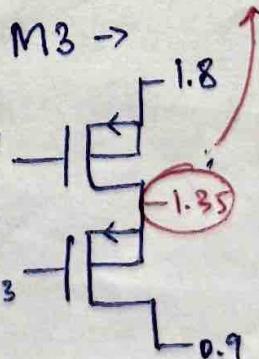

$$\begin{aligned} V_{q_3} &= V_s - V_{Th} - 5\% V_{DD} \\ &= 1.35 - 500 \text{ mV} - 90 \text{ mV} \\ \therefore V_{q_3} &= 0.76 \text{ V} \end{aligned}$$

M4 \rightarrow

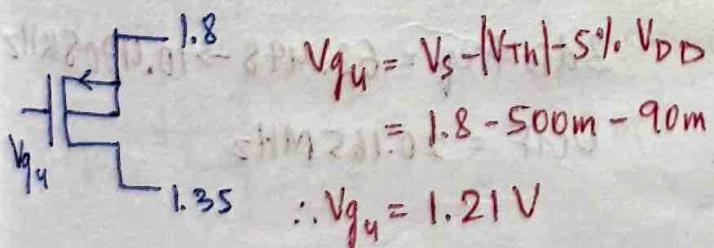


$$\begin{aligned} V_{q_4} &= V_s - V_{Th} - 5\% V_{DD} \\ &= 1.8 - 500 \text{ mV} - 90 \text{ mV} \\ \therefore V_{q_4} &= 1.21 \text{ V} \end{aligned}$$

Perform DC analysis \rightarrow Select the respective T^A \rightarrow Select simW \rightarrow
 Start = 2 μ m, Stop = 50 μ m (NMOS) \rightarrow Run
 Stop = 100 μ m (PMOS)

Outputs \rightarrow M1 \rightarrow Drain of M1 M3 \rightarrow Source of M4
 M2 \rightarrow Drain of M1 M4 \rightarrow Source of M4

Now, check w at $I = 100 \mu A$

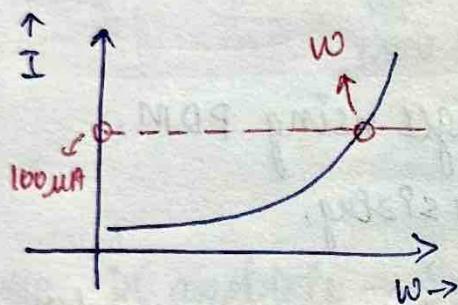


$$M1 = 14.946 \mu m$$

$$M2 = 16.65 \mu m$$

$$M3 = 41.475 \mu m \text{ (Make Fingers = 1)}$$

$$M4 = 77.345 \mu m \text{ (Make Fingers = 2)}$$

Now, connect the ckt. as.

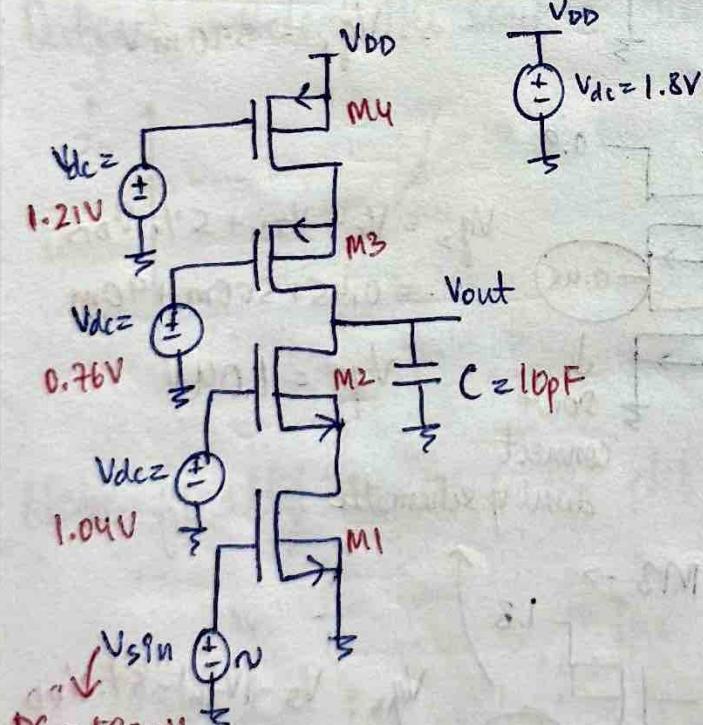


$$AC mag = 1V$$

$$Amp = 1mV$$

$$freq = 1 \text{ kHz}$$

Now, AC analysis \rightarrow freq = 1 to 100Hz

Output \rightarrow Vout net

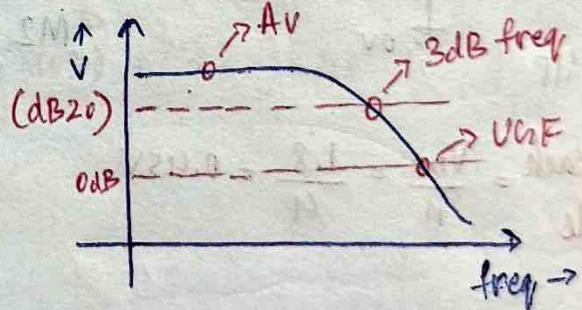


$$\therefore AV(dB) = 65.498$$

$$3 \text{dB freq} = 62.498 \rightarrow 10.4708 \text{ kHz}$$


$$UCRF = 20.165 \text{ MHz}$$

AICD - Exp 4c


Transistor sizing :-

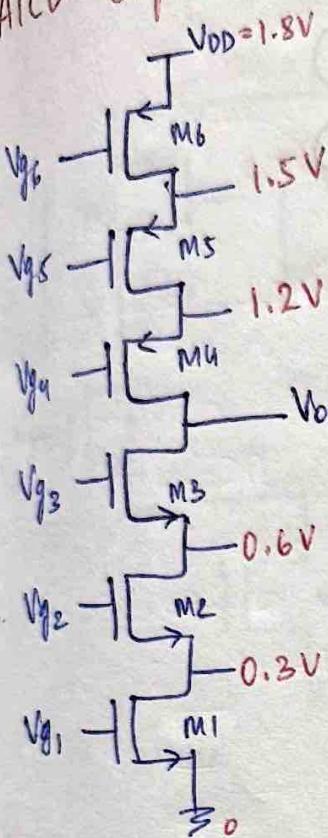

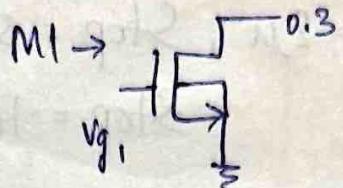
$$V \text{ at each node} = \frac{V_{DD}}{n} = \frac{1.8}{6} = 0.3 \text{ V}$$



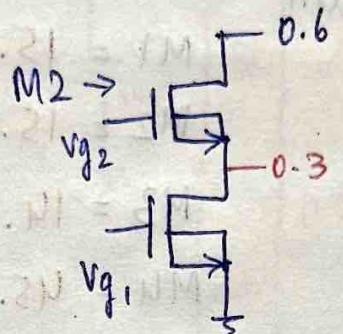
$$\begin{aligned} V_{g1} &= V_s + V_{Th} + 5\% V_{DD} \\ &= 0 + 500m + 90m \\ &= 590 \text{ mV} \end{aligned}$$



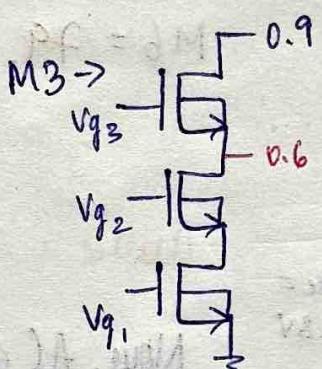
$$\begin{aligned} V_{g2} &= V_s + V_{Th} + 5\% V_{DD} \\ &= 0.3 + 500m + 90m \\ &= 890 \text{ mV} \end{aligned}$$



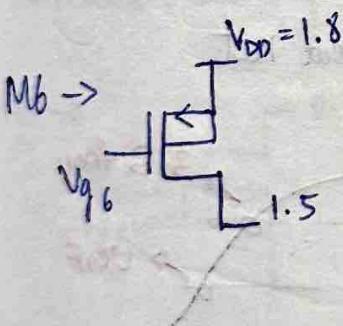
$$\begin{aligned} V_{g3} &= V_s + V_{Th} + 5\% V_{DD} \\ &= 0.6 + 500m + 90m \\ &= 1.19 \text{ V} \end{aligned}$$



$$\begin{aligned} V_{g6} &= V_s - |V_{Th}| - 5\% V_{DD} \\ &= 1.8 - 500m - 90m \\ &= 1.21 \text{ V} \end{aligned}$$

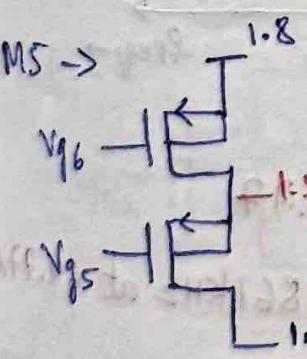

$$\begin{aligned} V_{g5} &= V_s - |V_{Th}| - 5\% V_{DD} \\ &= 1.5 - 500m - 90m \\ &= 910 \text{ mV} \end{aligned}$$

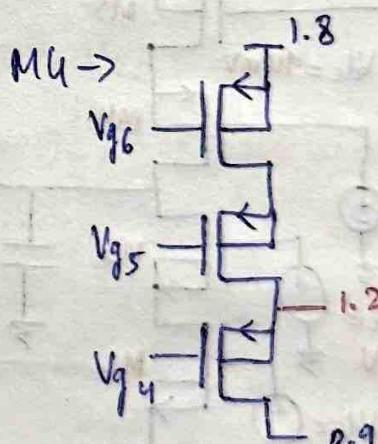


$$\begin{aligned} V_{g4} &= V_s - |V_{Th}| - 5\% V_{DD} \\ &= 1.2 - 500m - 90m \\ &= 610 \text{ mV} \end{aligned}$$

Outputs → For M1, M2, M3 → Drain of M1
For M4, M5, M6 → Source of M6

For DC analysis \rightarrow Select the $T^M \rightarrow$ Select simW (width) \rightarrow
 Start = 2μ , Stop = 50μ (NMOS)
 Stop = 100μ (PMOS)

Now, check w at $I = 100\mu A$

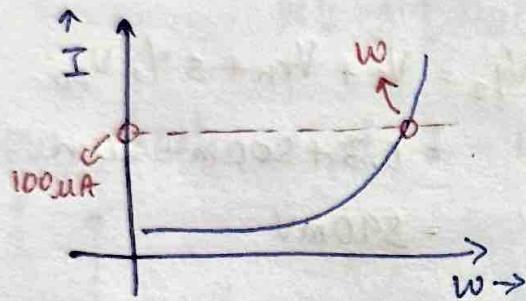

$$M_1 = 15.31\mu m$$

$$M_2 = 15.4\mu m$$


$$M_3 = 14.87\mu m$$

$$M_4 = 45.36\mu m$$

$$M_5 = 52.94\mu m$$


$$M_6 = 79.18\mu m$$

Now, connect the ckt. as,

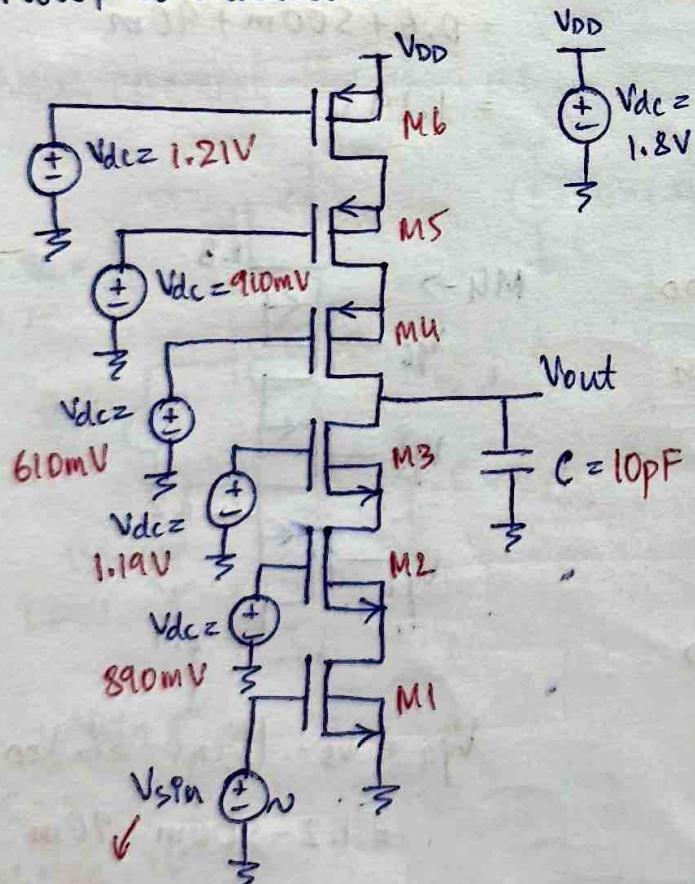

Now, AC analysis \rightarrow freq = 1 to 1 GHz

Output \rightarrow $V_{out\ net}$

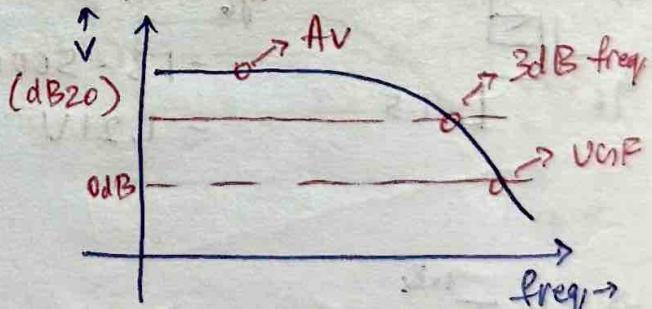

$$\therefore Av(dB) = 67.77$$

$$3\text{dB freq} = 7.861\text{ kHz at } 64.77\text{ dB}$$

$$UGF = 19.69\text{ MHz}$$


$$DC\ voltage = 590mV$$

$$AC\ mag = 1V$$

$$Amp = 1mV$$

$$freq = 1\text{ kHz}$$

AICD - Exp 5

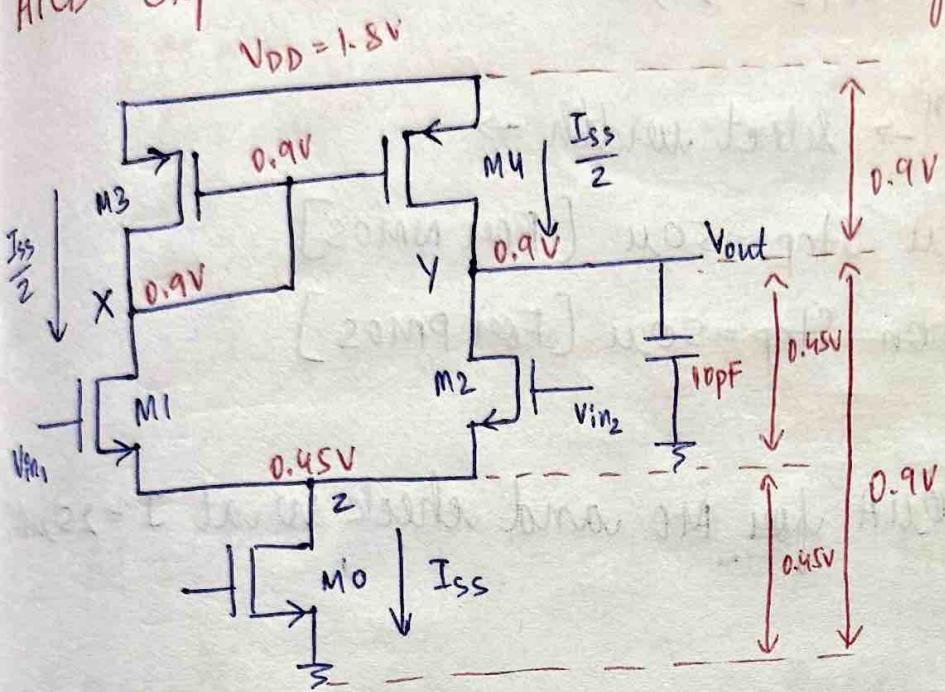

Using PDM,

$$1) V_{DD} = 1.8V$$

$$2) V_X = V_Y = V_{out} = 0.9V$$

$$V_{g3} = V_{g4} = V_X = 0.9V$$

$$3) V_Z = 0.45V$$

Length = 3 times 180nm
 $\approx 500nm$


$$\text{Now, } I_{SS} = \text{Slew rate} \times C_L$$

$$\therefore \frac{I_{SS}}{2} = \frac{50\mu A}{2} = 25\mu A$$

$$= 5V/\mu\text{sec} \times 10\text{pF} = 5.0\mu A$$

Transistor sizing :-

M0 \rightarrow

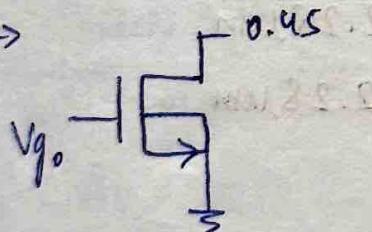


Now,

$$V_{g0} = V_s + V_{TH} + 5\% V_{DD}$$

$$= 0 + 500m + 90m = 590mV$$

M1, M2 \rightarrow

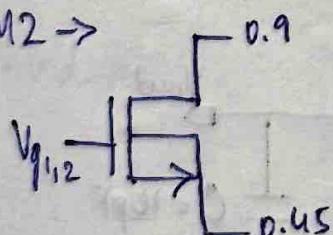


Now,

$$V_{g1,2} = V_s + V_{TH} + 5\% V_{DD}$$

$$= 0.45 + 500m + 90m = 1.04V$$

M3, M4 \rightarrow

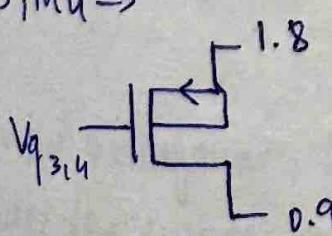

Now,

$$V_{g3,4} = 0.9V$$

[Because both PMOS are connected to node X &
 $V_X = 0.9V$]


$$W.K.T., I_{SS} = 50\mu A \quad \& \quad I_{SS}/2 = 25\mu A$$

DC analysis \rightarrow Select T^* \rightarrow Select width \rightarrow


$$Start = 2\mu \text{m} \quad Stop = 50\mu \text{m} \quad [\text{For NMOS}]$$

$$Start = 400\text{n} \quad Stop = 50\mu \text{m} \quad [\text{For PMOS}]$$

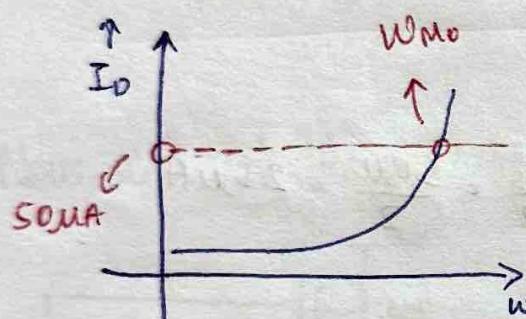Now, check w at $I = 50\mu A$ for M_0 and check w at $I = 25\mu A$ for M_1, M_2, M_3, M_4



$$w_0 = 9.68\mu \text{m}$$

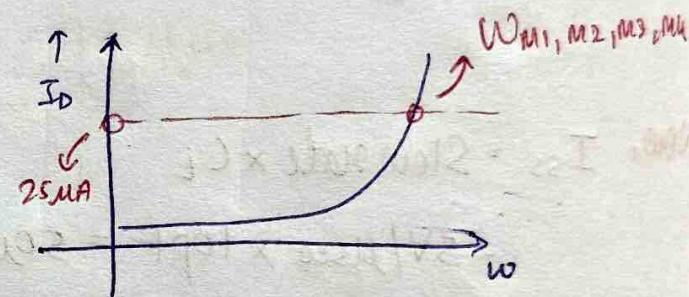


$$w_1 = 5.04\mu \text{m}$$

$$w_2 = 5.04\mu \text{m}$$

$$w_3 = 2.28\mu \text{m}$$

$$w_4 = 2.28\mu \text{m}$$

Now, connect the ckt. as,

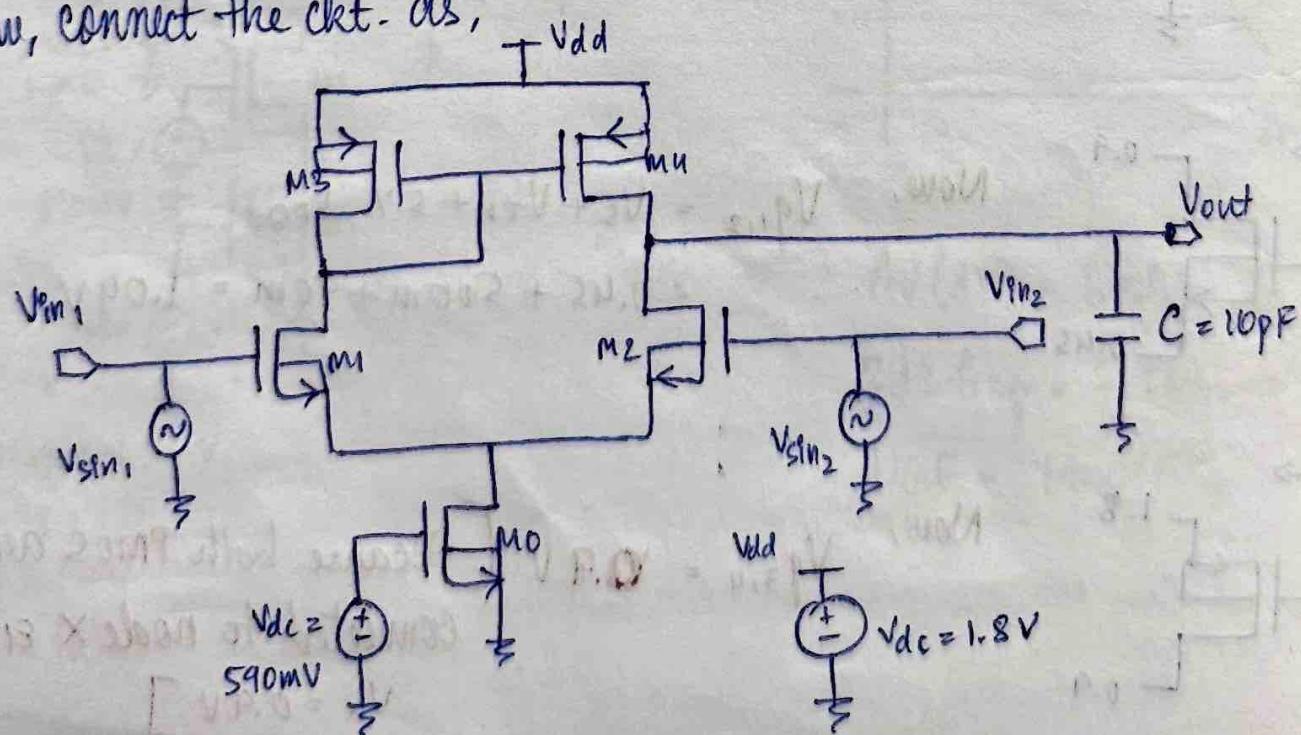

$V_{sin_1} \rightarrow$ DC voltage = 1.04V

AC mag = 1V

Amp = 1mV

f = 1KHz

AC phase = 0

Initial sinusoidal phase = 0

$V_{sin_2} \rightarrow$ DC voltage = 1.04V

AC mag = 1V


Amp = 1mV

f = 1KHz

AC phase = 180

Initial sinusoidal phase = 180

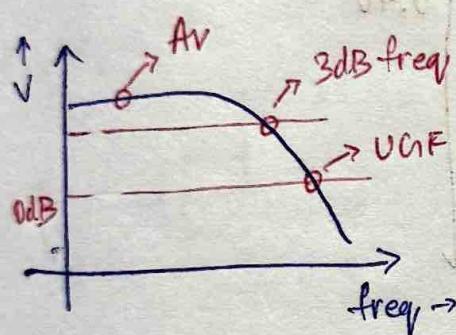Now, AC analysis \rightarrow freq = 1 to 10GHz Outputs $\rightarrow V_{out}$ net



$$\therefore AV(dB) = 42.83$$

3dB freq = 71.83 KHz at 39.83dB


UCF = 9.966 MHz

Transient \rightarrow Stop time = 10m

$$V_{o(p-p)} = 264.6 mV$$

$$V_{i(p-p)} = 1.965 mV$$
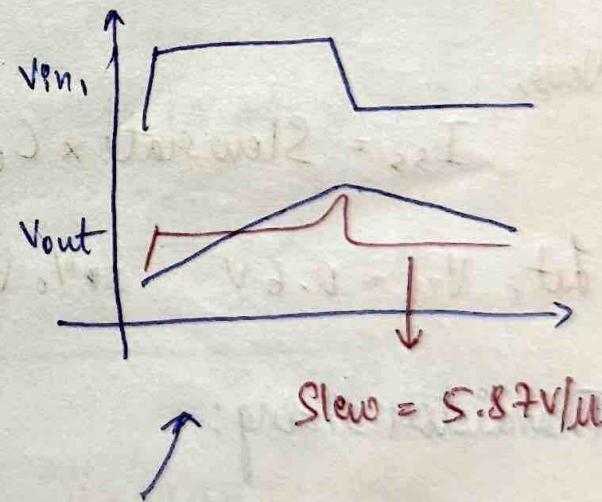
$$AV = \frac{V_{o(p-p)}}{V_{i(p-p)}} = \frac{264.6 m}{1.965 m} = 134.7$$



To find slew: - Transient \rightarrow Stop time = 20n

Now replace V_{sin} with V_{pulse} \rightarrow DC voltage = 1.04V,


Period = 20n, Pulse width = 10n

$$V_{sin_1} \rightarrow V_1 = 0V \quad \& \quad V_2 = 1.8V$$

$$V_{sin_2} \rightarrow V_1 = 1.8V \quad \& \quad V_2 = 0V$$

In the waveform, select the V_{out} wave \rightarrow Apply derive function \rightarrow Now Place the cursor on the new wave to get slew value.

AICD - Exp 6

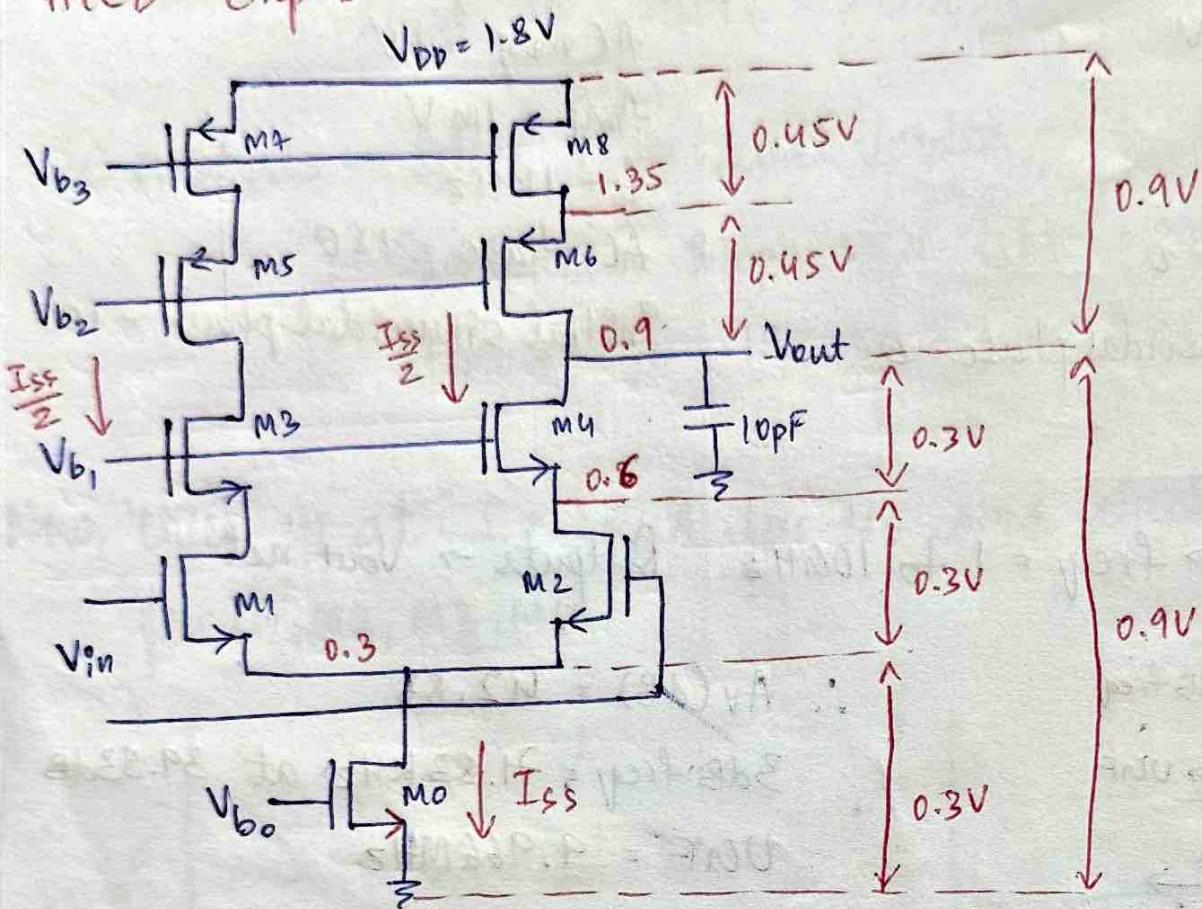

Now,


$$I_{ss} = \text{Slew rate} \times C_L = 5V/\mu s \times 10pF = 50\mu A$$

Let, $V_{TH} = 0.6V$ $50\% V_{DD} = 90mV$ $L = 3 \text{ times } 180n \approx 500nm$

Transistor sizing:-

$$\frac{I_{ss}}{2} = 25\mu A$$


$M_0 \rightarrow$

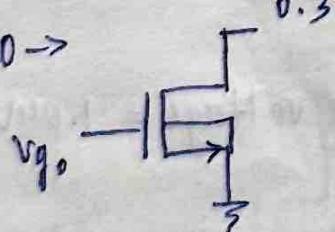

$$V_{g0} = V_s + V_{TH} + 50\% V_{DD}$$


$$= 0 + 600m + 90m = 690mV$$

$M_1, M_2 \rightarrow$

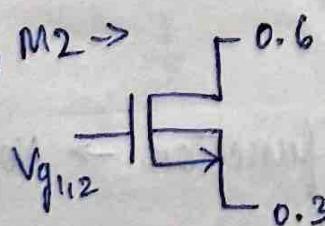


$$V_{g1,2} = V_s + V_{TH} + 50\% V_{DD}$$

$$= 0.3 + 600m + 90m = 990mV$$

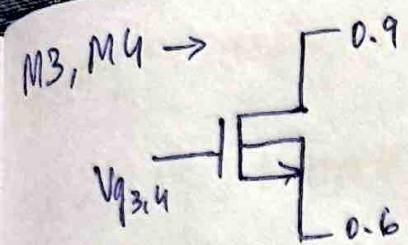


$$V_{g_{3,4}} = V_s + V_{Th} + 5\% \cdot V_{DD}$$

$$= 0.6 + 600m + 90m = 1.29V$$

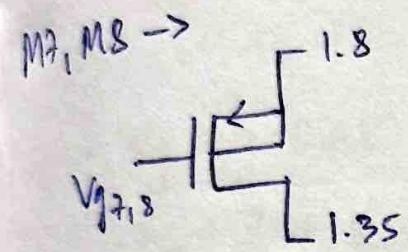

$$V_{g_{7,8}} = V_s - |V_{Th}| - 5\% \text{ of } V_{DD}$$


$$= 1.8 - 600m - 90m = 1.11V$$

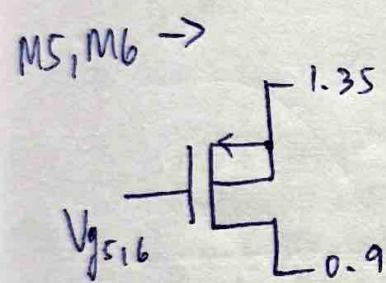

$$V_{g_{5,6}} = V_s - |V_{Th}| - 5\% \cdot V_{DD}$$


$$= 1.35 - 600m - 90m = 660mV$$

For $M_0 \rightarrow W$ at $I = 50\mu A$

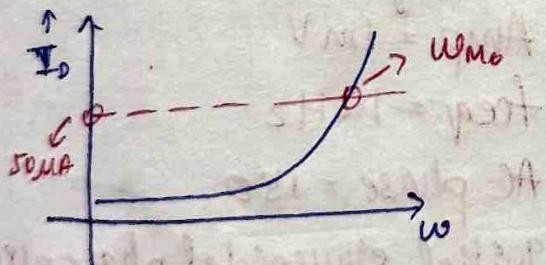

$$\therefore W_{M_0} = 3.54\mu m$$

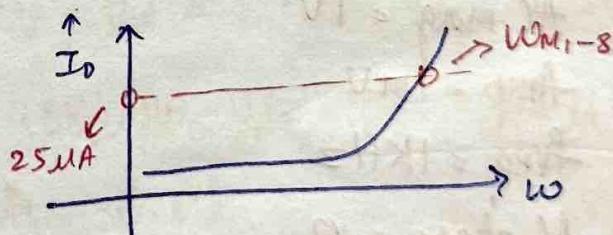For $M_1-8 \rightarrow W$ at $I = 25\mu A$



$$W_{M_1} = 1.699\mu m \approx 1.7\mu m$$

$$W_{M_2} = 1.699\mu m \approx 1.7\mu m$$

$$W_{M_3} = 1.7\mu m$$

$$W_{M_4} = 1.7\mu m$$

$$W_{M_5} = 7.288\mu m \approx 7.3\mu m$$

$$W_{M_6} = 7.3\mu m$$

$$W_{M_7} = 7.3\mu m$$


$$W_{M_8} = 7.3\mu m$$

DC analysis →

Start = 2μ Stop = 50μ (NMOS)

Start = 100μ Stop = 50μ (PMOS)


Now, connect the ckt. as,

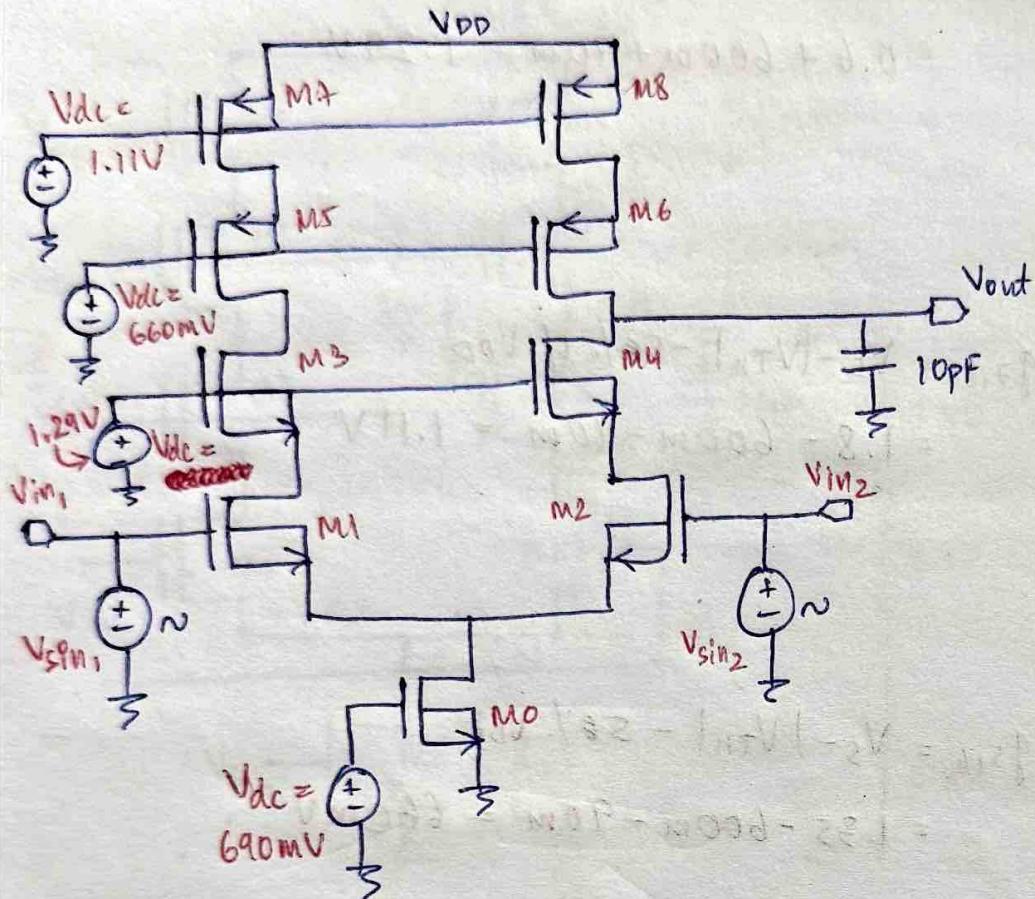

$V_{sin_1} \rightarrow$ DC voltage = 990mV
 AC mag = 1V
 Amp = 1mV
 freq = 1KHz
 AC phase = 0
 initial sinusoidal phase = 0

$V_{sin_2} \rightarrow$ DC voltage = 990mV
 AC mag = 1V
 Amp = 1mV
 freq = 1KHz
 AC phase = 180
 initial sinusoidal phase = 180

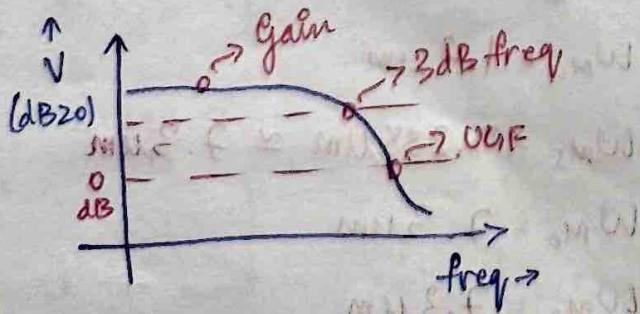Now, AC analysis \rightarrow freq = 1 to 10kHz Output \rightarrow V_{out} net



$$\therefore Av(\text{dB}) = 50.57$$

3dB freq = 8.39 kHz at 47.57 dB

UGF = 2.932 MHz

Dummy DC analysis

M0 $\rightarrow V_g = 690\text{mV}$, $V_s = 0\text{V}$, $V_d = 300.195\text{mV}$, $V_b = 0\text{V}$,
 $I_D = 50.0054\mu\text{A}$, $g_m = 412.793\mu\text{A/V}$, $g_{ds} = 15.185\mu\text{A/V}$,
 $R_o = 65.854\text{k}\Omega$, Self gain = $g_m R_o = 27.18$

M1 $\rightarrow V_g = 990\text{mV}$, $V_s = 300.195\text{mV}$, $V_d = 604.938\text{mV}$,
M2 $V_b = 300.195\text{mV}$, $I_D = 25.0025\mu\text{A}$, $g_m = 202.672\mu\text{A/V}$,
 $g_{ds} = 7.65529\mu\text{A/V}$, $R_o = 130.629\text{k}\Omega$, Self gain = 26.47

M3 $\rightarrow V_g = 1.29\text{V}$, $V_s = 604.938\text{mV}$, $V_d = 1.13557\text{V}$,
M4 $V_b = 604.938\text{mV}$, $I_D = 25.0059\mu\text{A}$, $g_m = 209.521\mu\text{A/V}$,
 $g_{ds} = 2.75484\mu\text{A/V}$, $R_o = 362.998\text{k}\Omega$, Self gain = 76.05


M5 $\rightarrow V_g = 660\text{mV}$, $V_s = 1.36037\text{V}$, $V_d = 1.13\text{V}$, $V_b = 1.36037\text{V}$,
M6 $I_D = 24.9992\mu\text{A}$, $g_m = 163.488\mu\text{A/V}$, $g_{ds} = 26.9048\mu\text{A/V}$,
 $R_o = 37.1681\text{k}\Omega$, Self gain = 6.07

M7 $\rightarrow V_g = 1.11\text{V}$, $V_s = 1.8\text{V}$, $V_d = 1.36037\text{V}$, $V_b = 1.8\text{V}$,
M8 $I_D = 25.0027\mu\text{A}$, $g_m = 184.681\mu\text{A/V}$, $g_{ds} = 3.47763\mu\text{A/V}$,
 $R_o = 287.552\text{k}\Omega$, Self gain = 53.10

Transient \rightarrow Stop time = 20 ns

For transient analysis, replace the V_{sin} with $V_{pulse} \rightarrow$
DC voltage = 990mV, Period = 20ns, Pulse width = 10ns,
for $V_{SPN1} \rightarrow V_1 = 0V \& V_2 = 1.8V$
for $V_{SPN2} \rightarrow V_1 = 1.8V \& V_2 = 0V$

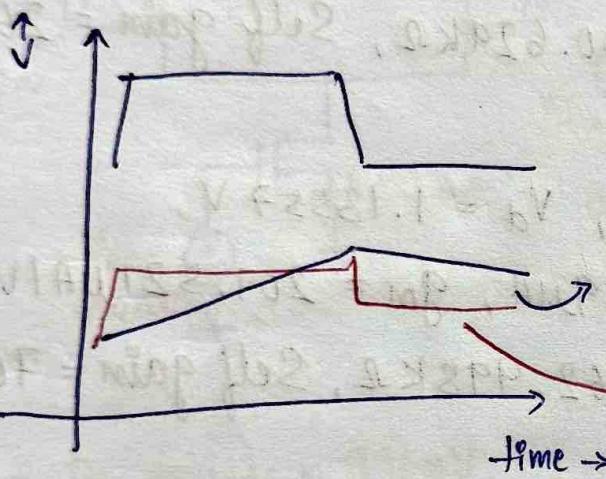Outputs \rightarrow Select V_{out} & V_{in} , \rightarrow Run the analysis



In calculator, select the wave & apply the deriv function, we get a new wave, place cursor on that wave
 $\therefore \text{Slew} = 2.5031 \text{ V/us}$


Transient \rightarrow with V_{sin}

$$V_o(p-p) = 2 \text{ mV}$$

$$V_o(p-p) = 489.5 \text{ mV}$$

$$AV = \frac{V_o(p-p)}{V_i(p-p)} = \frac{489.5 \text{ m}}{2 \text{ m}} = 244.75$$

AICD - Exp 7

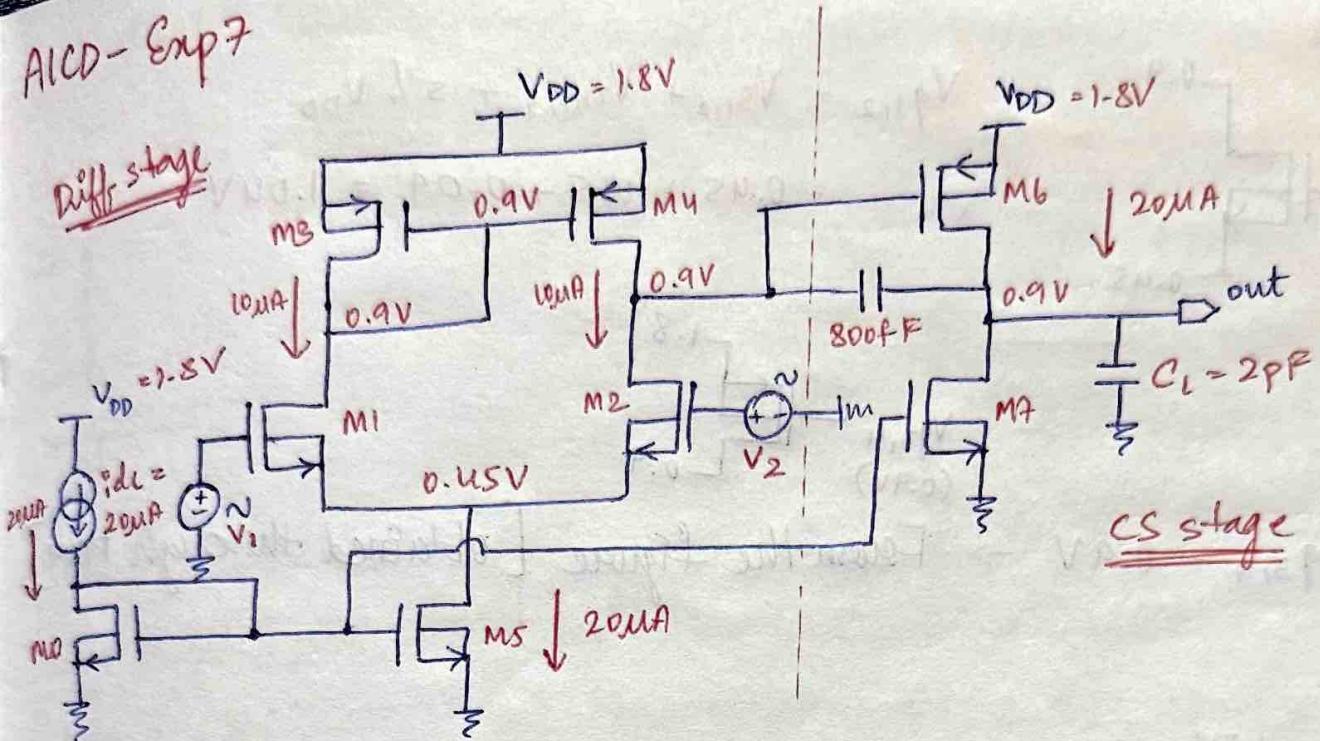

Given $V_{DD} = 1.8V$

Slew rate = $20V/\mu s$

$$C_L = 2 \text{ pF}$$

$$V_{Th} = 0.5 \text{ V} = 500 \text{ mV}$$

$$\begin{aligned} \text{Now, } I_{ss} &= C_L \times \text{Slew rate} \\ &= 2 \times 20 \times 10^{-6} = 40 \mu\text{A} \end{aligned}$$


Here, we have two stages :-

- 1) Diff stage
- 2) CS stage

So, each stage carries $I = 20 \mu\text{A}$

Transistor sizing :-


M5 :-

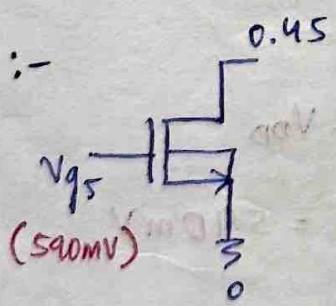

$$\begin{aligned} V_{gs} &= V_{ss5} + V_{Th5} + 5\% V_{DD} \\ &= 0 + 500 \text{ mV} + 90 \text{ mV} = 590 \text{ mV} \end{aligned}$$

DC analysis \rightarrow Select NMOS \rightarrow Select size \rightarrow Start = 100n, Stop = 50μ \rightarrow Outputs \rightarrow Select drain of NMOS \rightarrow Run \rightarrow Check w at $I = 20 \mu\text{A}$


M1, M2 :-

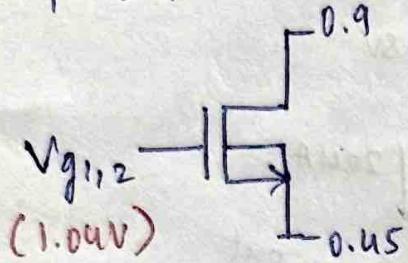

$$V_{g1,2} = V_{S1,2} + V_{Th1,2} + 5\% \cdot V_{DD}$$


$$= 0.45 + 0.5 + 0.09 = 1.04V$$

M3, M4 :-

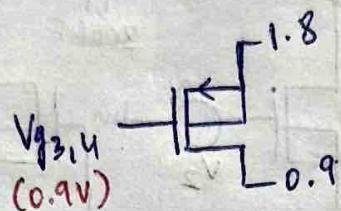

$V_{g3,4} = 0.9V \rightarrow$ From the figure [obtained through PDM]


M0 :-

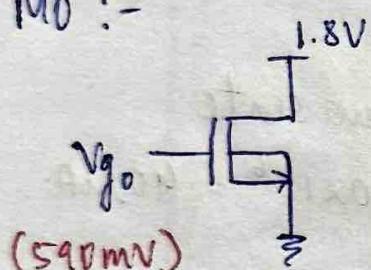

$$V_{g0} = V_{S0} + V_{Th0} + 5\% \cdot V_{DD}$$

$$= 0 + 500m + 90m = 590mV$$

M6 :-

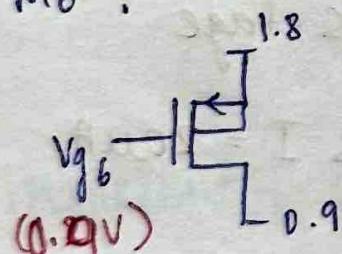


~~$$V_{g6} = V_{S6} + V_{Th6} + 5\% \cdot V_{DD}$$~~

$$V_{g6} = 0.9V$$

From the
figure

M7 :-

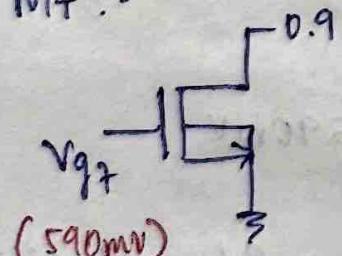


$$V_{g7} = V_{S7} + V_{Th7} + 5\% \cdot V_{DD}$$

$$= 0 + 500m + 90m = 590mV$$

Now, in DC curve,

$w = ?$ at $I = 20\text{mA}$

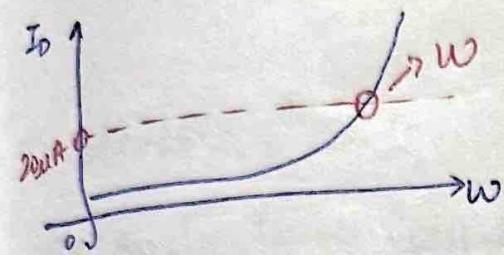


$$w_0 = 3.56\mu\text{m}$$

$$w_5 = 3.99\mu\text{m}$$

$$w_6 = 1.83\mu\text{m}$$

$$w_7 = 3.81\mu\text{m}$$

$w = ?$ at $I = 10\text{mA}$

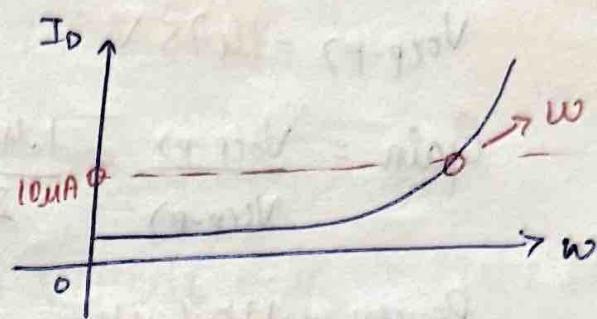

$$w_1 = 1.88\mu\text{m}$$

$$w_2 = 1.88\mu\text{m}$$

$$w_3 = 922.93\text{nm} \approx 925\text{nm}$$

$$w_4 = 922.93\text{nm} \approx 925\text{nm}$$

Now,

V1 \rightarrow DC voltage = 1.04V

AC mag = 1V

freq = 1KHz

Amp = 1mV

AC phase = 0

initial sinusoidal phase = 0

V2 \rightarrow DC voltage = 1.04V

AC mag = 1V

freq = 1KHz

Amp = 1mV

AC phase = 180

initial sinusoidal phase = 180

Now,

AC analysis \rightarrow freq = 1 to 10Hz Output \rightarrow out net

\therefore Gain (dB) = 70.04

3dB freq = 14.863KHz at 67.04 dB

UCF = 24.186MHz

Transient \rightarrow Stop time = 10ms Outputs \rightarrow V₁, V₂ & out net

$$V_{i(P-P)} = 2 \text{ mV}$$

$$V_{o(P-P)} = 1.475 \text{ V}$$

$$\text{Gain} = \frac{V_{o(P-P)}}{V_{i(P-P)}} = \frac{1.475}{2 \text{ m}} = 737.5$$

$$\text{Power} = 110.6 \mu\text{W}$$

M1, M2 \rightarrow V_g = 1.04V, V_s = 442.69mV, V_d = 877.386mV,
V_b = 442.69mV, I_D = 10.946mA, g_m = 137.946μA/V,
g_{ds} = 1.49687μA/V, g_t = 668.062kΩ, Self gain = 92.156

M3, M4 \rightarrow V_g = 877.386mV, V_s = 1.8V, V_d = 877.386mV, V_b = 1.8V,
I_D = 10.946mA, g_m = 40.923μA/V, g_{ds} = 719.819μA/V,
g_t = 1.389MΩ, Self gain = 56.85


M5 \rightarrow V_g = 596.99mV, V_s = 0V, V_d = 442.69mV, V_b = 0V,
I_D = 21.89mA, g_m = 281.595μA/V, g_{ds} = 2.86042μA/V,
g_t = 349.599kΩ, Self gain = 98.44

M6 \rightarrow V_g = 877.386mV, V_s = 1.8V, V_d = 870.899mV, V_b = 1.8V,
I_D = 21.847mA, g_m = 81.9952μA/V, g_{ds} = 1.4343μA/V,
g_t = 697.201kΩ, Self gain = 57.167

$\text{mA} \rightarrow V_g = 596.99\text{mV}$, $V_s = 0\text{V}$, $V_d = 870.899\text{mV}$, $V_b = 0\text{V}$,
 $I_D = 21.847\text{mA}$, $g_m = 278.97\text{mA/V}$, $g_{ds} = 1.748\text{mA/V}$,
 $g_o = 572.066\text{k}\Omega$, Self gain = 159.587

To calculate phase:-

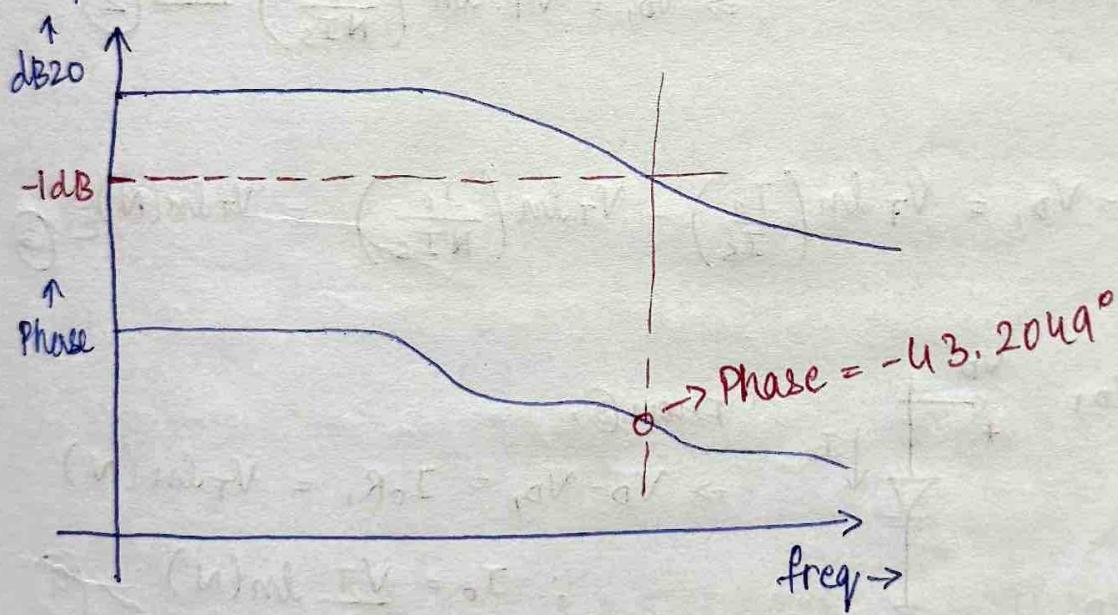AC analysis \rightarrow Copy the AC curve to separate strip \rightarrow Make one waveform to dB20 \rightarrow Make the other to type "Phase" \rightarrow None in the dB20 plot place a horizontal line at -1dB . \rightarrow Place a vertical line and at the intersection point, check value of phase in the Phase plot.




Now,

$$\text{Phase Margin} = 180 - 43.2049 = 136.79^\circ$$

AICD - Exp 8

$$V_{DD} = 3.3V \quad I_{DC} = 5mA \quad N = 2 \quad (\text{For PTAT})$$


CTAT :-

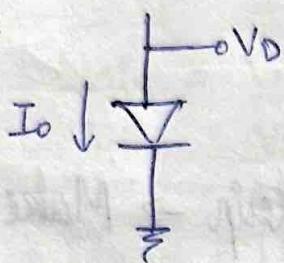

$$I_o = I_s e^{V_D/V_T}$$

$$\therefore V_D = V_T \cdot \ln\left(\frac{I_o}{I_s}\right) \quad \text{--- (1)}$$

PTAT :-

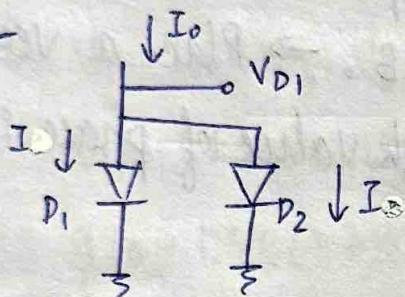

$$I_o = NI \quad \text{W.K.T., } I = I_s e^{V_{D1}/V_T}$$


$$\therefore I_o = N \cdot I_s e^{V_{D1}/V_T}$$

$$\Rightarrow V_{D1} = V_T \cdot \ln\left(\frac{I_o}{NI_s}\right) \quad \text{--- (2)}$$

Now,

$$(1) - (2) \Rightarrow V_D - V_{D1} = V_T \ln\left(\frac{I_o}{I_s}\right) - V_T \ln\left(\frac{I_o}{NI_s}\right) = V_T \ln(N) \quad \text{--- (3)}$$

Now,

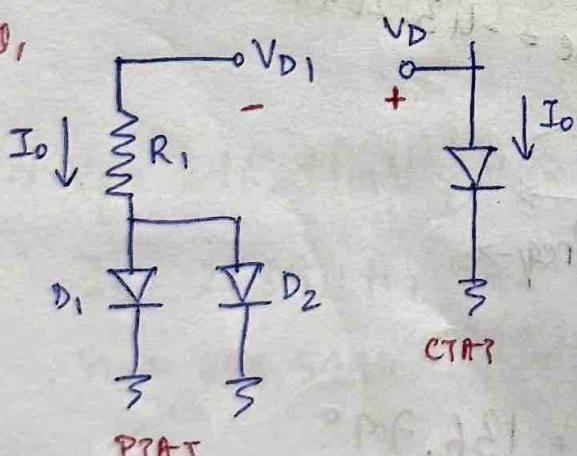

From (3),


$$\Rightarrow V_D - V_{D1} = I_o R_1 = V_T \ln(N)$$

$$\therefore I_o = \frac{V_T \ln(N)}{R_1} \quad \text{--- (4)}$$

(*)

$$R_1 = \frac{V_T \ln(N)}{I_o}$$

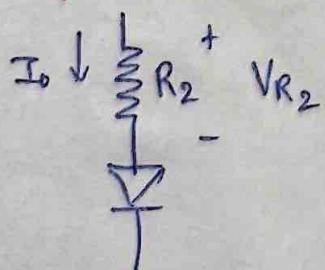For getting PTAT, consider a separate resistor, therefore



$$\therefore V_{R2} = I_o R_2 = V_T \ln(N) \frac{R_2}{R_1} \rightarrow \text{From (4)}$$

$$\therefore V_{R2} = \alpha_1 V_T \quad \text{where, } \alpha_1 = \ln(N) \frac{R_2}{R_1}$$

$$\text{W.K.T, } V_{\text{ref}} = \alpha_1 V_T + \alpha_2 V_D$$

$$= \alpha_1 V_T + \alpha_2 V_D - \textcircled{5}$$

$$\text{Now, } \frac{\partial V_{\text{ref}}}{\partial T} = 0 \Rightarrow \alpha_1 \frac{\partial V_T}{\partial T} + \alpha_2 \frac{\partial V_D}{\partial T} = 0$$

$$\therefore \alpha_1 (0.086 \text{ mV/K}) + \alpha_2 (-1.6 \text{ mV/K}) = 0$$

Assume, $\alpha_2 = 1$

$$\therefore \alpha_1 = \frac{1.6}{0.086} = 18.60$$


$$\textcircled{5} \Rightarrow \therefore V_{\text{ref}} = (18.6)(26 \text{ m}) + (1)(0.7) = 1.1836 \approx 1.2 \text{ V}$$

$$\text{Now, W.K.T, } R_1 = \frac{V_T \ln(N)}{I_0} = \frac{(26 \times 10^{-3}) \ln(2)}{5 \times 10^{-6}} = 3.6 \text{ k}\Omega$$

$$\text{W.K.T, } \alpha_1 = \ln(N) \frac{R_2}{R_1} \Rightarrow R_2 = \frac{\alpha_1 R_1}{\ln(N)}$$


$$\therefore R_2 = \frac{(18.6)(3.6 \times 10^3)}{\ln(2)} = 96.6 \text{ k}\Omega$$

Note :- Rig up the circuit in 90nm tech

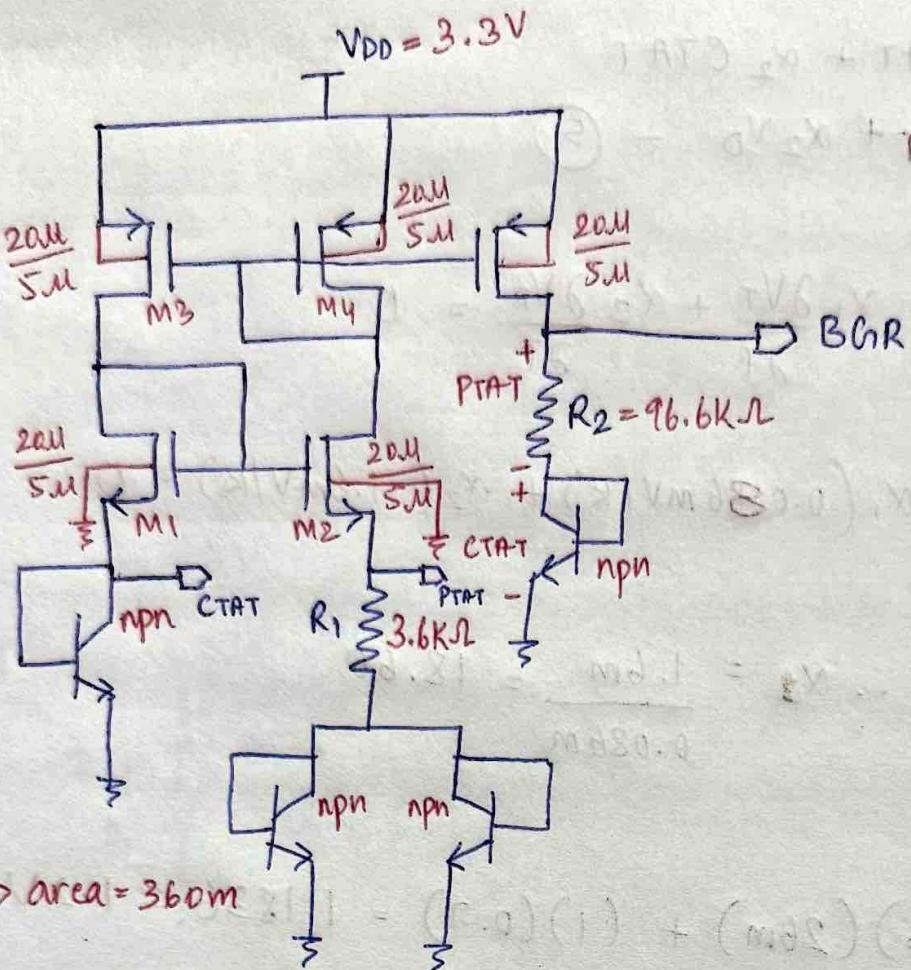


- 1) DC analysis :- Select Temperature \rightarrow Start = -50 Stop = 125
Outputs \rightarrow Select CTAT, PTAT, BGR
Extract graphs separately & at last one graph will all three pins

AICD - Exp 9

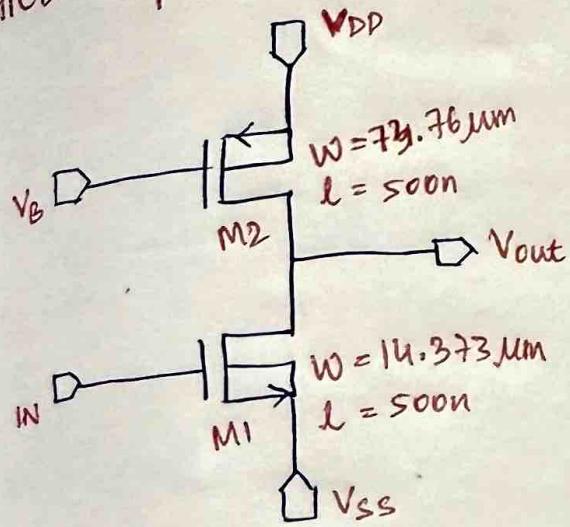


Perform transistor sizing :-

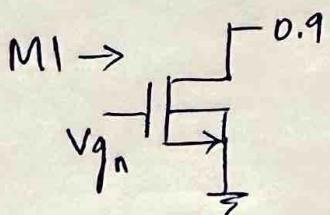

$$V_{g_n} = V_s + V_{Th} + 5\% V_{DD}$$

$$= 0 + 500m + 90m$$

$$\therefore V_{g_n} = 590mV$$

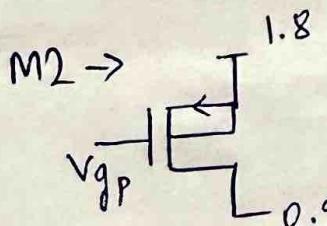

$$V_{gp} = V_s - |V_{Th}| - 5\% V_{DD}$$


$$= 1.8 - 500m - 90m$$

$$\therefore V_{gp} = 1.21V$$

DC analysis \rightarrow Select component \rightarrow Select PMOS/NMOS \rightarrow
Select simw (simulation width) \rightarrow Start = 400n, Stop = 100μ \rightarrow OK

Outputs \rightarrow Drain of NMOS & Source of PMOS (Do separately)
 \hookrightarrow For NMOS & PMOS

Now, w = ? at I = 100mA

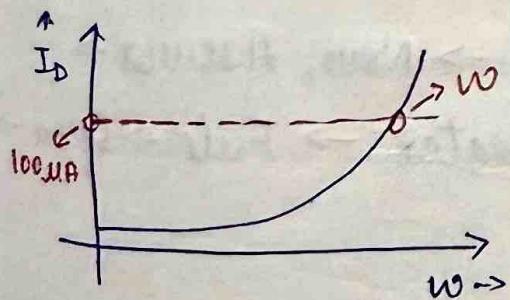

$$\therefore W_p = 73.76 \mu m$$

$$W_N = 14.373 \mu m$$


Note:- For 180nm tech, max width of device = 50μ. If the width exceeds 50μ, use fingers = 2.

\therefore For PMOS \rightarrow Fingers = 2

$$F \cdot W = 36.88 \mu m$$


$$T \cdot W = 73.76 \mu m$$

Dummy DC analysis \rightarrow M2 & M1

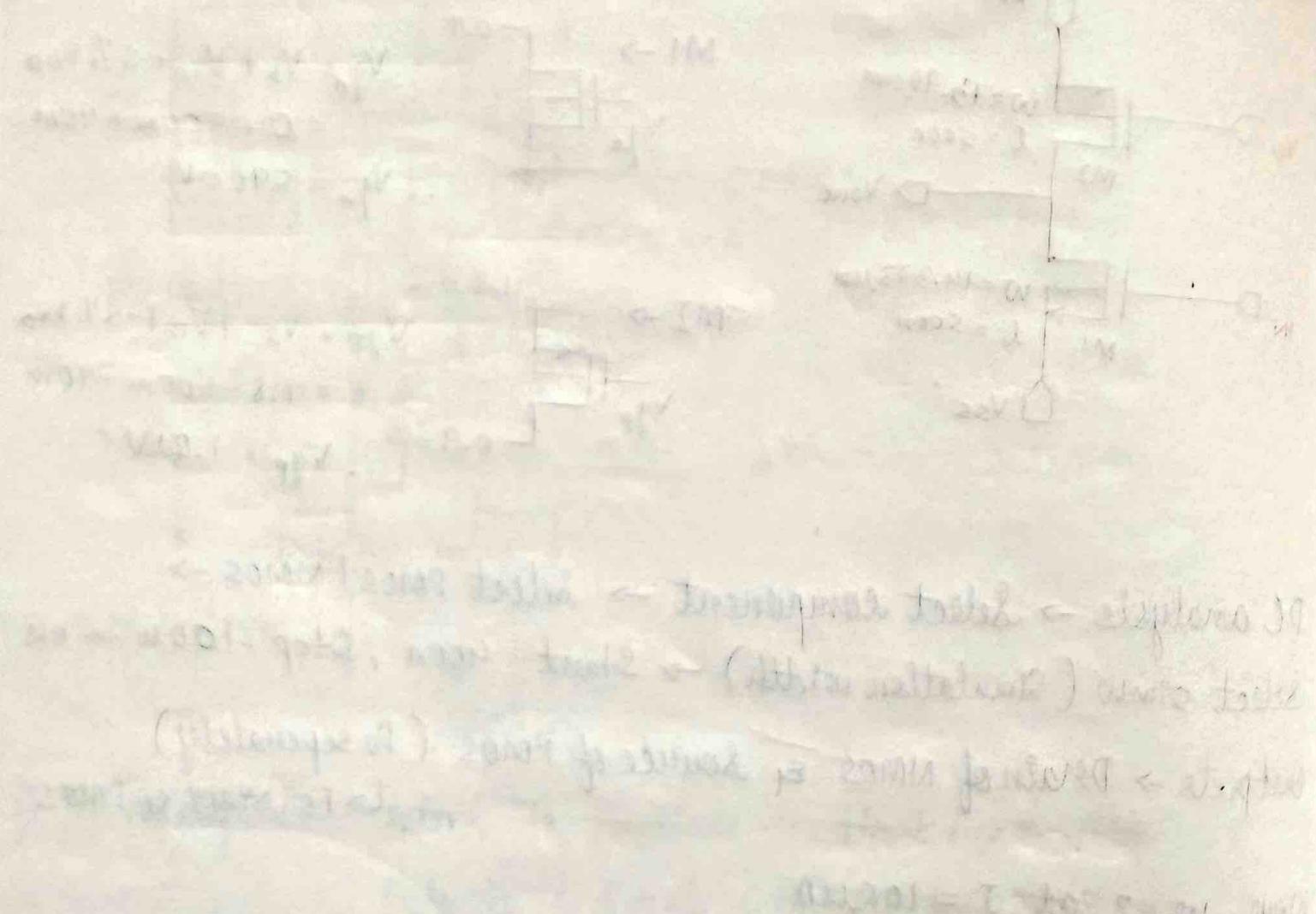

After layout creation \rightarrow Clear DRC & LVS \rightarrow New, Assemble \rightarrow Run Quantus \rightarrow After av-extracted is created \rightarrow File \rightarrow Open \rightarrow View \rightarrow av-extracted \rightarrow Click OK

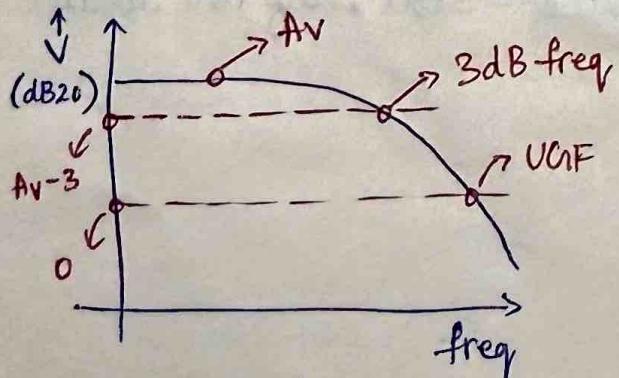Per layout AC analysis \rightarrow freq = 1 to 16Hz Output \rightarrow Vout



$$\text{Gain(dB)} = 37.84$$

$$3\text{dB freq} = 252.51 \text{ kHz at } 34.84 \text{ dB}$$

$$\text{VCIF} = 20.153 \text{ MHz}$$


Transient \rightarrow Stop time = 10m Output $\rightarrow V_{in}$ & V_{out}

$$V_{o(P-P)} = 155.6 \text{ mV}$$

$$V_{i(P-P)} = 2 \text{ mV}$$

$$\text{Gain} = \frac{V_{o(P-P)}}{V_{i(P-P)}} = \frac{155.6 \text{ m}}{2 \text{ m}} = 77.8$$

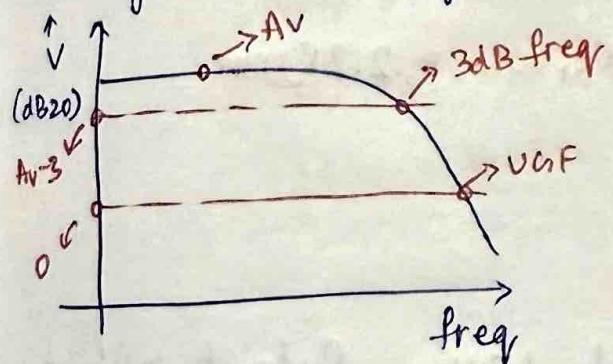Post layout AC analysis \rightarrow freq = 1 to 1 GHz Output $\rightarrow V_{out}$



$$\text{Gain(dB)} = 37.74$$

$$3\text{dB freq} = 246.856 \text{ kHz at } 34.74 \text{ dB}$$

$$VCF = 19.4827 \text{ MHz}$$


Post layout transient \rightarrow Stop time = 10m Output $\rightarrow V_{in}$ & V_{out}

$$V_{o(P-P)} = 154 \text{ mV}$$

$$V_{i(P-P)} = 2 \text{ mV}$$

$$\text{Gain} = \frac{V_{o(P-P)}}{V_{i(P-P)}} = \frac{154 \text{ m}}{2 \text{ m}} = 77$$

AICD - Exp 10

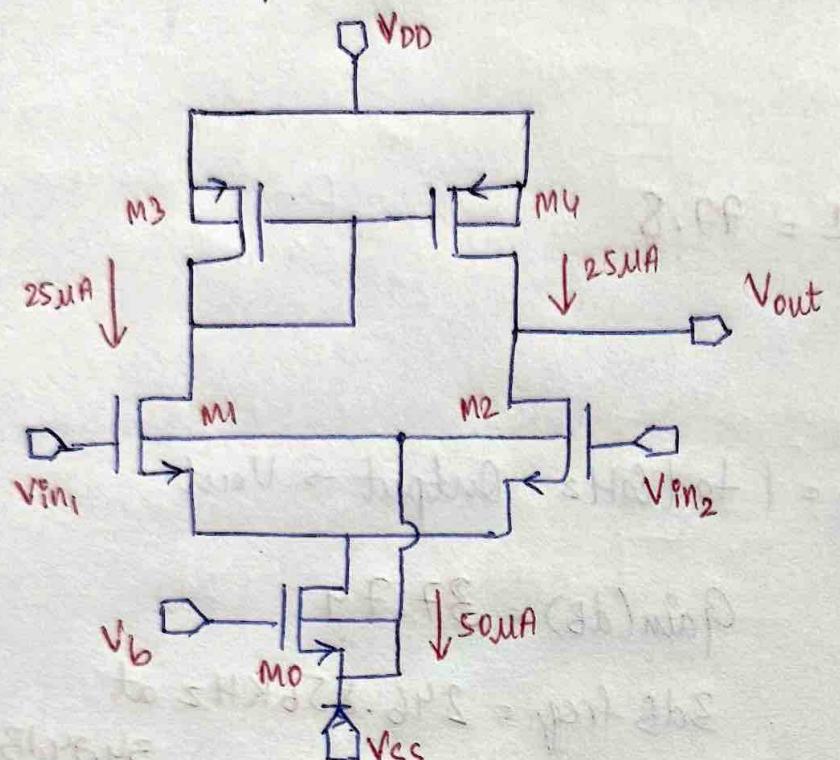

Perform Transistor sizing
(For simplicity, take the results of Exp-5)


$$L = 500\text{ nm}$$

$$W_0 = 9.68\text{ }\mu\text{m}$$

$$W_1, W_2 = 5.04\text{ }\mu\text{m}$$

$$W_3, W_4 = 2.28\text{ }\mu\text{m}$$

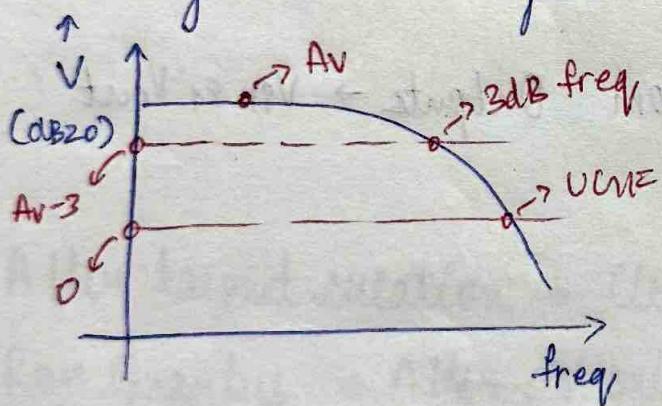Post layout AC analysis :- freq = 1 to 1 GHz Output $\rightarrow V_{\text{out}}$



$$\text{Gain (dB)} = 42.83$$

$$3\text{dB freq} = 71.83\text{ kHz at } 39.83\text{ dB}$$

$$V_{\text{CF}} = 9.966\text{ MHz}$$

Post layout AC analysis :-

$$\text{Gain (dB)} = 43.14$$

$$3\text{dB freq} = 66.943\text{ kHz at } 40.14$$

$$V_{\text{CF}} = 9.9597\text{ MHz}$$

Pre layout transient \rightarrow Stop time = 10m Output $\rightarrow V_{in}, \epsilon_1, V_{out}$

$$V_{o(P-P)} = 264.6 \text{ mV}$$

$$V_{i(P-P)} = 1.965 \text{ mV}$$

$$\text{Gain} = \frac{V_{o(P-P)}}{V_{i(P-P)}} = 134.7$$

Post layout transient \rightarrow

$$V_{o(P-P)} = 271.8 \text{ mV}$$

$$V_{i(P-P)} = 1.946 \text{ mV}$$

$$\text{Gain} = \frac{V_{o(P-P)}}{V_{i(P-P)}} = 139.7$$

Dummy DC analysis $\rightarrow M_0, M_1 \& M_2, M_3 \& M_4$